



ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)

Vadhiraj K P P

Department of Electrical Engineering

ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)


Unit 2 – Lecture 24 - Analysis of Single-Phase AC circuits with C Load

Vadhiraj K P P

Department of Electrical & Electronics Engineering

Capacitor & the concept of Capacitance

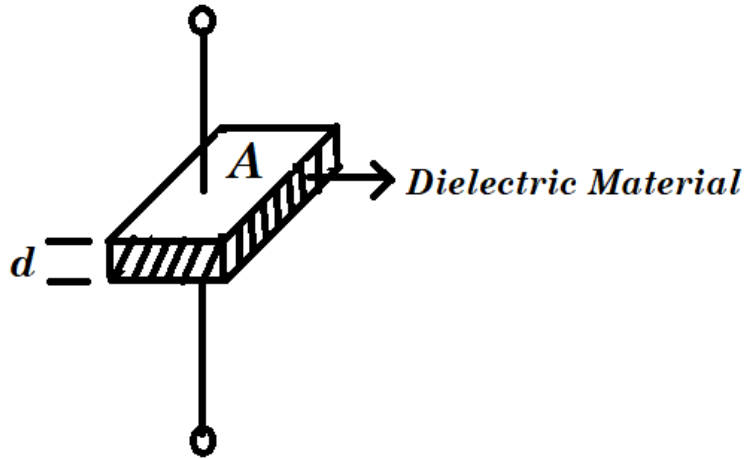A Capacitor is obtained by placing a dielectric medium between the conducting plates.




$$\text{Capacitance, } C = \frac{\epsilon A}{d} \text{ Farad}$$

Where, A is the area of each of the plates in m^2

d is the distance between the plates in m

ϵ is the permittivity of the dielectric medium in F/m

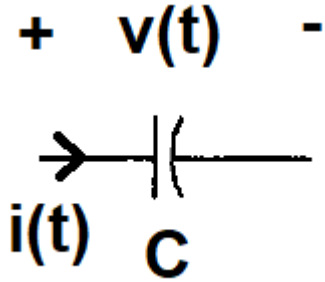Voltage – Current relationship in a Capacitor



The charge on the plates of a capacitor is directly proportional to the voltage across its terminals.

$$\text{i.e., } q(t) \propto v(t) \Rightarrow q(t) = Cv(t)$$


The constant of proportionality 'C' is called Capacitance of the Capacitor.

$$\text{Hence, current, } i(t) = \frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$$

Therefore, $v(t)$ can be expressed as

$$v(t) = \frac{1}{C} \int i(t) dt$$

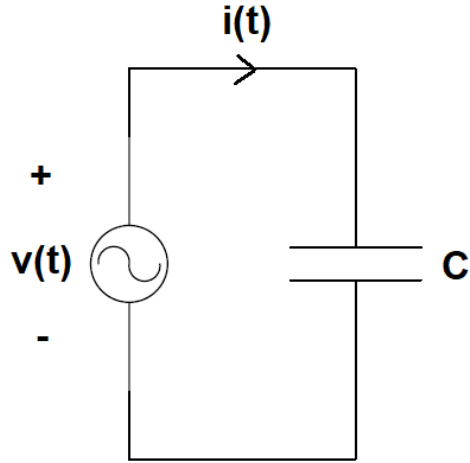Response of Pure Capacitor to Sinusoidal Supply




Let the supply voltage be $v(t) = V_m \sin(\omega t)$

$$\begin{aligned}\text{In a pure capacitor, } i(t) &= C \frac{dv(t)}{dt} \\ &= CV_m \omega \cos(\omega t) \\ &= I_m \sin(\omega t + 90^\circ)\end{aligned}$$

Where, $I_m = V_m \omega C$ is the peak value of current

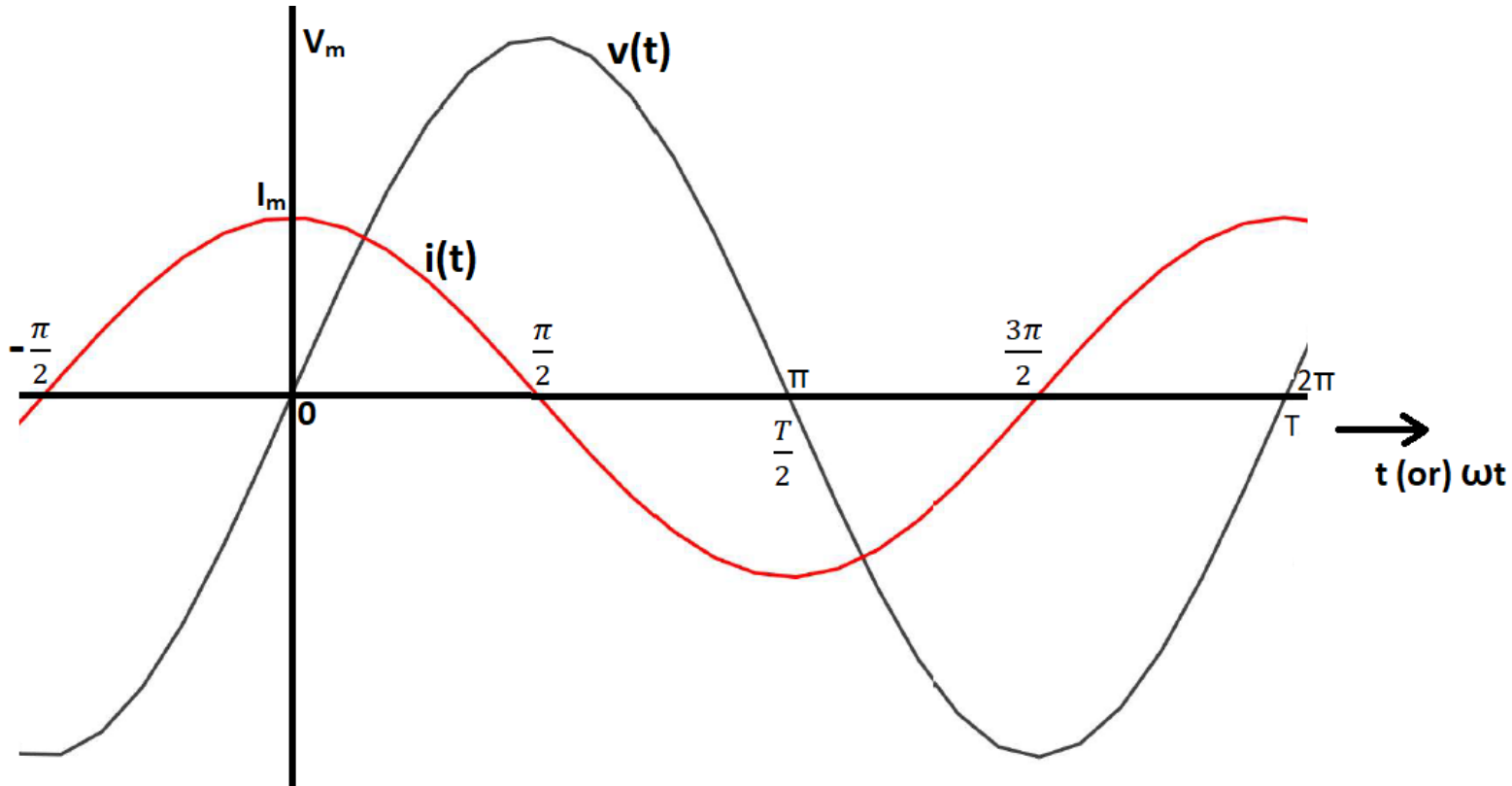Response of Pure Capacitor to Sinusoidal Supply




In a pure capacitor, current **leads** voltage by 90°

Response of Pure Capacitor to Sinusoidal Supply

$$v(t) = V_m \sin(\omega t) \Rightarrow \bar{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$

$$i(t) = I_m \sin(\omega t + 90^\circ) \Rightarrow \bar{I} = \frac{I_m}{\sqrt{2}} \angle 90^\circ$$

Phasor Diagram:

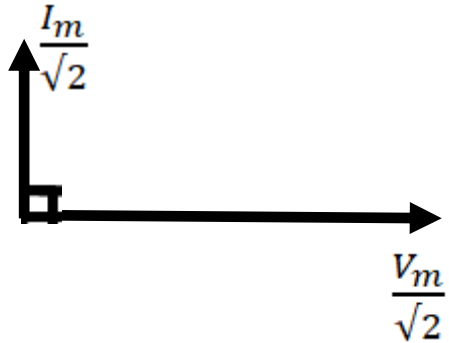

$$Z = \frac{\bar{V}}{\bar{I}} = \frac{\frac{V_m}{\sqrt{2}} \angle 0^\circ}{\frac{I_m}{\sqrt{2}} \angle 90^\circ} = \frac{1}{\omega C} \angle -90^\circ = -jX_c \quad \Omega$$

Where, $X_c = \frac{1}{\omega C}$ is called '**Capacitive Reactance**'

Numerical Example

Question:

A Capacitor of Capacitance $100\mu\text{F}$ is connected across an AC voltage source $100\sin(100\pi t)$ V. Determine

- i) Capacitive Reactance
- ii) Impedance
- iii) Instantaneous expression for the current

Also, draw the phasor diagram.

Numerical Example

Solution: Given, $V(t) = 100\sin(100\pi t)$ V

Hence, $\omega = 100\pi$ rad/s

i) Capacitive Reactance, $X_C = \frac{1}{\omega C} = 31.83\Omega$


ii) Impedance, $Z = -jX_C = -j31.83\Omega$

iii) Instantaneous current, $i(t) = V_m \omega C \sin(\omega t + 90^\circ)$ A
 $= 3.14\sin(\omega t + 90^\circ)$ A

Phasor Diagram:

$$\bar{V} = \frac{100}{\sqrt{2}} \angle 0^\circ \text{ V}$$
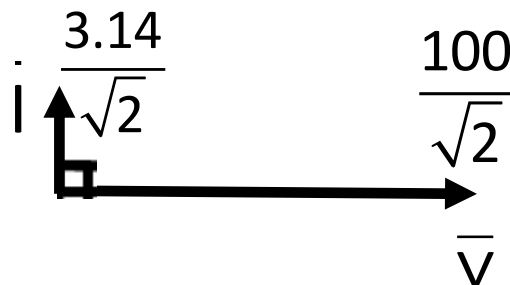
$$\bar{i} = \frac{3.14}{\sqrt{2}} \angle 90^\circ \text{ A}$$



Text Book & References

Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11th Edition, Pearson Education, 2012.

Reference Books:

1. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
2. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8th Edition, McGraw-Hill, 2012.



THANK YOU

Vadhiraj K P P

Department of Electrical & Electronics Engineering

vadhirajkpp@pes.edu