



# ELEMENTS OF ELECTRICAL ENGINEERING

## UE24EE141B

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

# **ELEMENTS OF ELECTRICAL ENGINEERING**

## **UE24EE141B**

---

### **Lecture 1 - Network Terminology & Basic Concepts**

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

## Network Terminology

---

### **Electrical Network:**

An interconnection of electrical elements.

### **Electrical Circuit:**

An electrical network with at least one source and a sink and having a closed path for current flow.

## Network Terminology

---

### **Active Element:**

An element which supplies or delivers energy in an electrical network.

Eg: Voltage Sources & Current Sources

### **Passive Element:**

An element which absorbs or stores energy in an electrical network.



Eg: Resistors, Inductors & Capacitors

## Electric Current

An electric current is defined as the rate of flow of charges across the cross section of a conductor.

It is given by,  $I = \frac{Q}{t}$  (or)  $i = \frac{dq}{dt}$

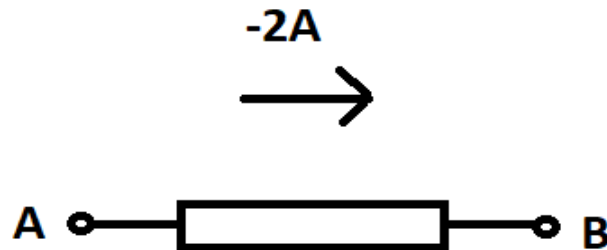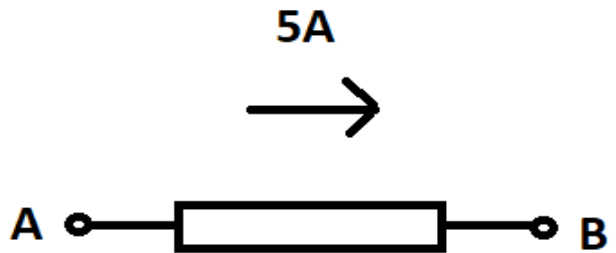It is measured in Amperes (A) & 1 Ampere = 1 Coulomb/sec




## Potential Difference


The energy required to move unit positive charge from one terminal to another is defined as the potential difference between the terminals.

It is given by,  $V = \frac{W}{Q}$

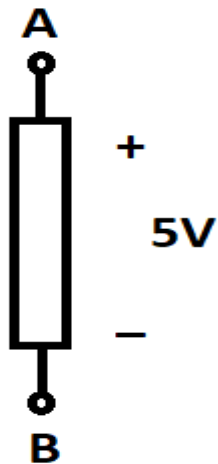It is measured in Volts (V) & 1 Volt = 1 Joule/Coulomb




## Double Subscript Notation for Voltage

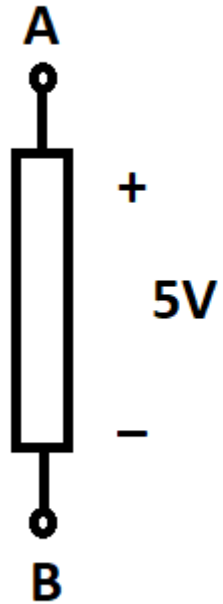


(a)

$$V_{AB} = 5V$$

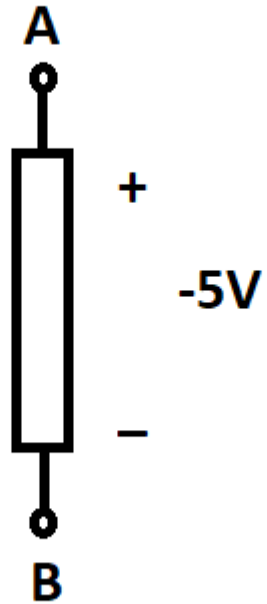

(b)

$$V_{AB} = -5V$$

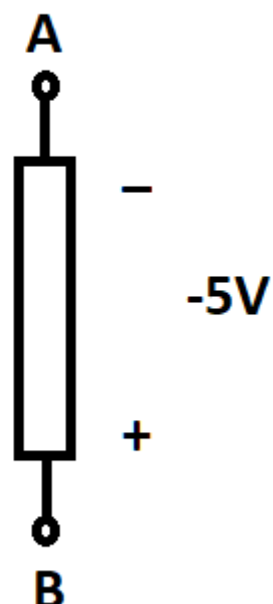

(c)



$$V_{AB} = 5V$$

## Electric Power

The rate of absorption or delivery of Electrical energy is called Electrical Power.

It is given by,  $P = V \cdot I$

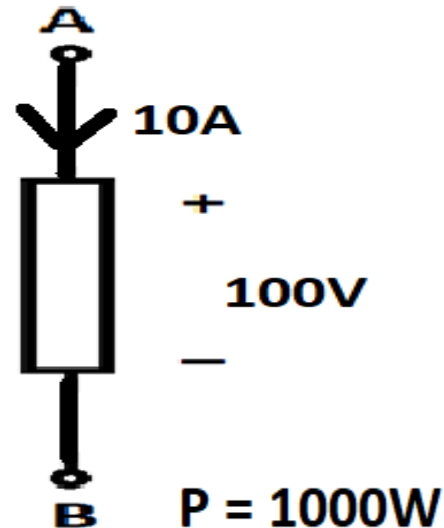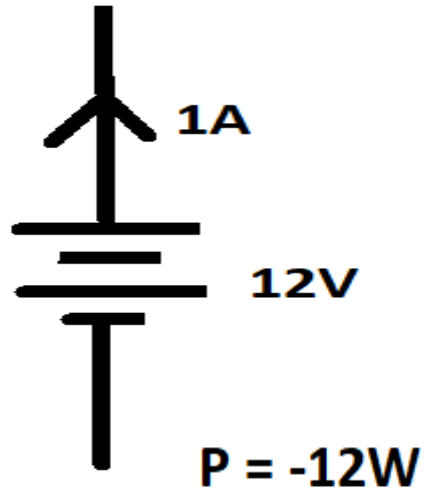It is measured in Watts (W) & 1 Watt = (1 Volt)\*(1 Ampere)





## Ohm's Law

---

At a constant temperature, the potential difference across the terminals of a conductor is directly proportional to the current flowing through it.

i.e.,  $V \propto I$

$$V = R \cdot I$$

Here,  $R$  is the electrical resistance of the conductor.

It is measured in Ohms ( $\Omega$ ) and 1 Ohm = 1 Volt/Ampere



## Ohm's Law

---

Resistance of a conductor is the opposition offered to the flow of current through it.

It depends on the resistivity of the material & its dimensions.

$$\text{i.e., } R = \frac{\rho l}{A}$$

Where,  $\rho$  is the resistivity measured in Ohm-m

$$\text{Conductance, } G = \frac{1}{R}$$

It is measured in Siemens (S)

## Active and Passive Sign Conventions

---

### Active sign convention:


Applicable to active elements

It says “current leaves positive terminal in an active element”.
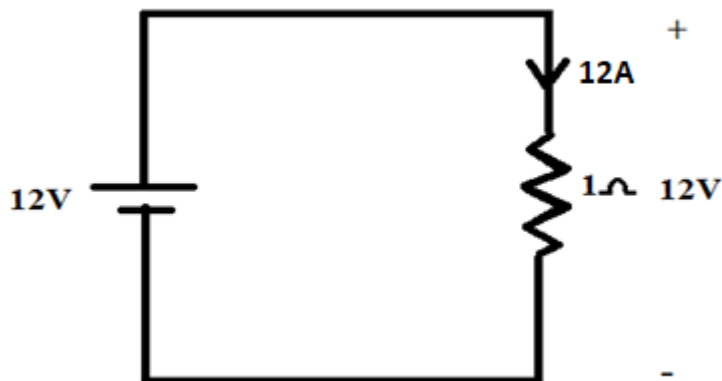
### Passive Sign Convention:

Applicable to passive elements

It says “current enters positive terminal in a passive element”.



## Text Book & References

---

### Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11<sup>th</sup> Edition, Pearson Education, 2012.

### Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8<sup>th</sup> Edition, McGraw-Hill, 2012.



**THANK YOU**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**