



# **ELEMENTS OF ELECTRICAL ENGINEERING**

## **UE24EE141B**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

# **ELEMENTS OF ELECTRICAL ENGINEERING**

## **UE24EE141B**

---


### **Lectures 4 & 5 - Voltage & Current Division Rules; Concept of Short Circuit & Open Circuit**

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

## Voltage Division Rule

It is applicable to Series Networks

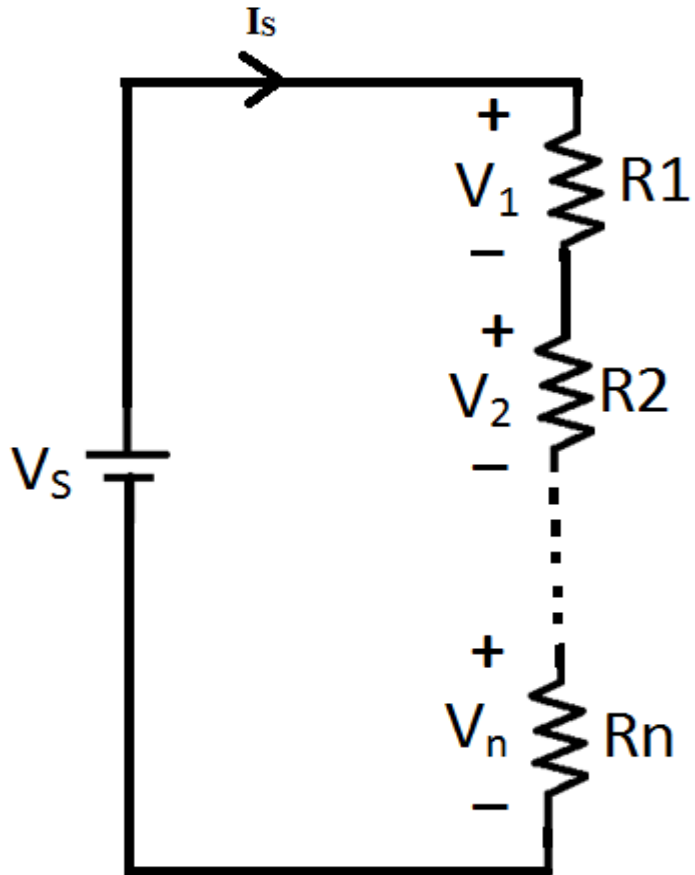

$$V_1 = I_S * R_1$$

$$V_2 = I_S * R_2$$

.

.


.

$$V_n = I_S * R_n$$

By KVL,

$$V_S = V_1 + V_2 + \dots + V_n$$

## Voltage Division Rule

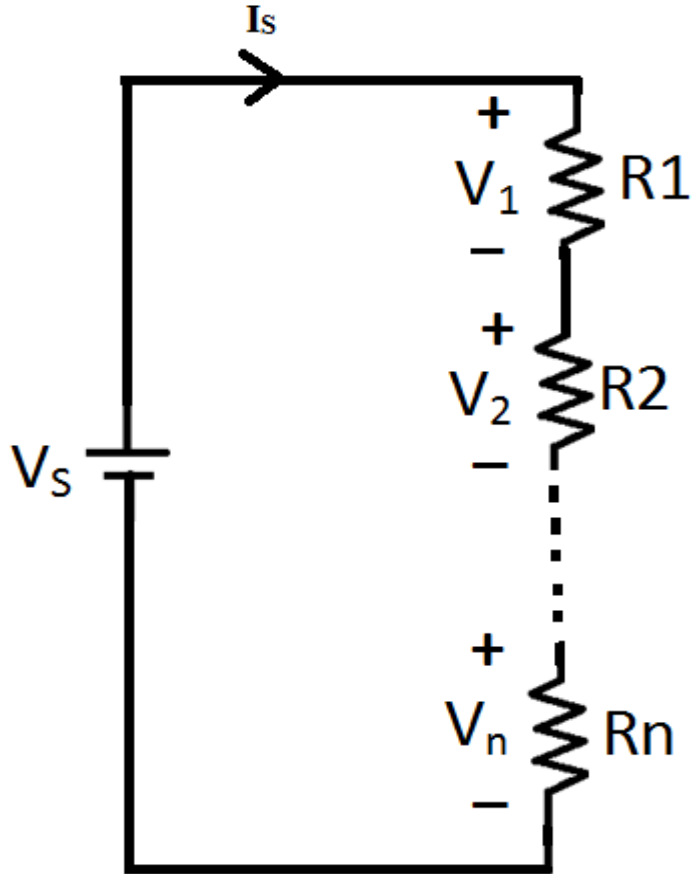

$$\text{Hence, } I_S = \frac{V_S}{(R_1 + R_2 + \dots + R_n)}$$

Therefore,


$$V_1 = \frac{V_S * R_1}{(R_1 + R_2 + \dots + R_n)}$$

.


.

$$V_n = \frac{V_S * R_n}{(R_1 + R_2 + \dots + R_n)}$$

## Equivalent Series Resistance

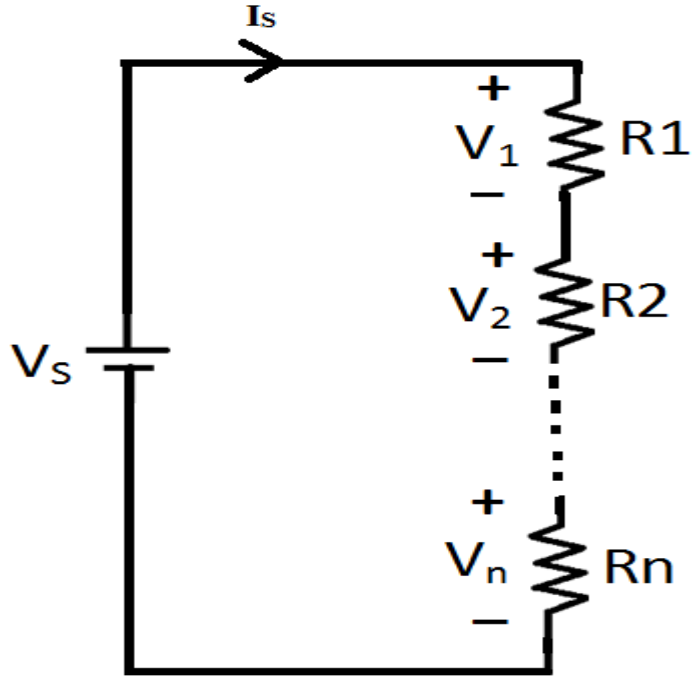
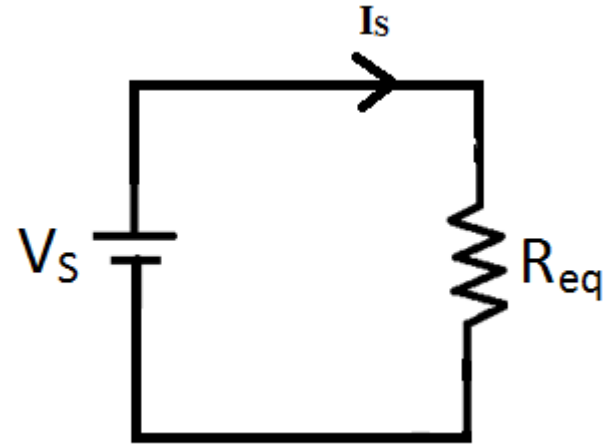
$$I_S = \frac{V_S}{(R_1 + R_2 + \dots + R_n)}$$




$$I_S = \frac{V_S}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

## Current Division Rule

It is applicable to Parallel Networks

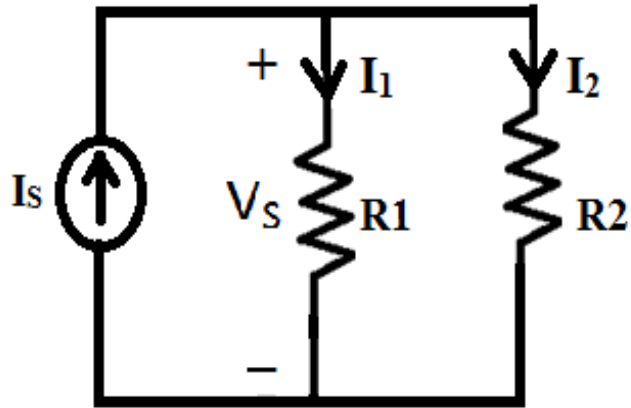

$$I_1 = \frac{V_S}{R_1}$$

$$I_2 = \frac{V_S}{R_2}$$


By KCL,

$$I_S = I_1 + I_2$$

$$I_S = V_S * \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

## Current Division Rule

---

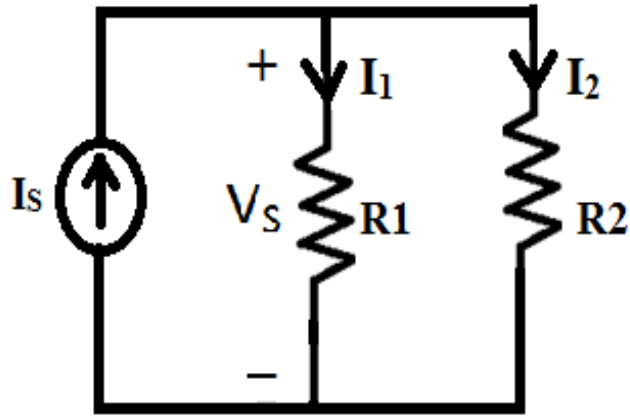


$$V_s = I_s * \frac{R_1 * R_2}{(R_1 + R_2)}$$

$$I_1 = I_s * \frac{R_2}{(R_1 + R_2)}$$

$$I_2 = I_s * \frac{R_1}{(R_1 + R_2)}$$

## Equivalent Parallel Resistance

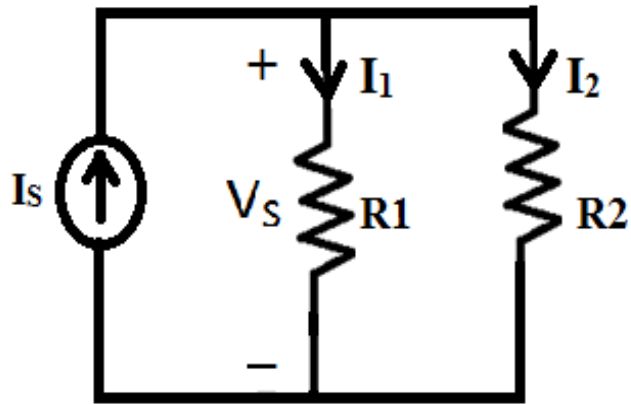


$$\frac{V_S}{I_S} = R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 * R_2}{(R_1 + R_2)}$$

In general, For n Resistors in Parallel,

$$\frac{1}{R_{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$



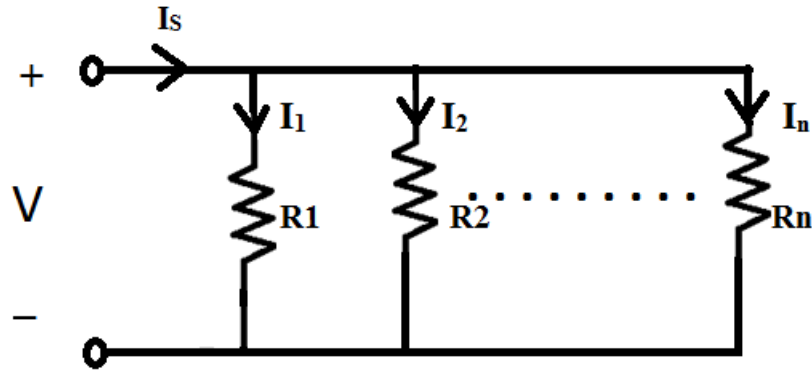
## Current Division Rule – More than two resistors in Parallel




- Obtain  $R_{eq}$  using
$$\frac{1}{R_{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$
- Find  $V$  using
$$V = I_S * R_{eq}$$
- Use Ohm's Law to find branch currents
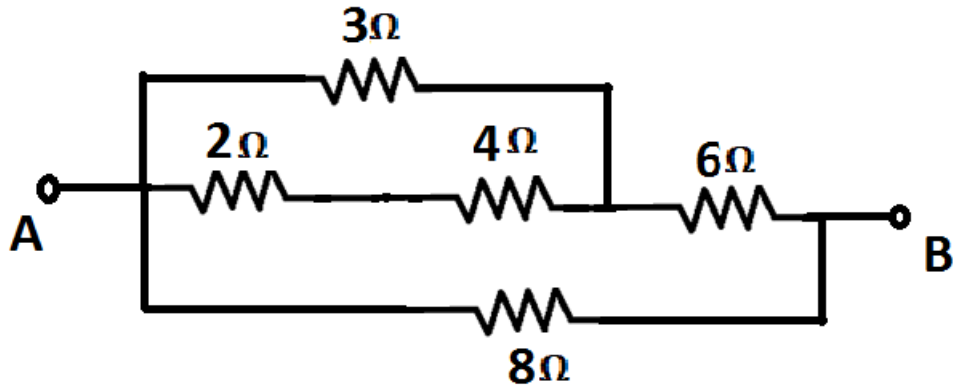
## Numerical Example – Finding Equivalent Resistance

Find the equivalent resistance between A & B






Solution:

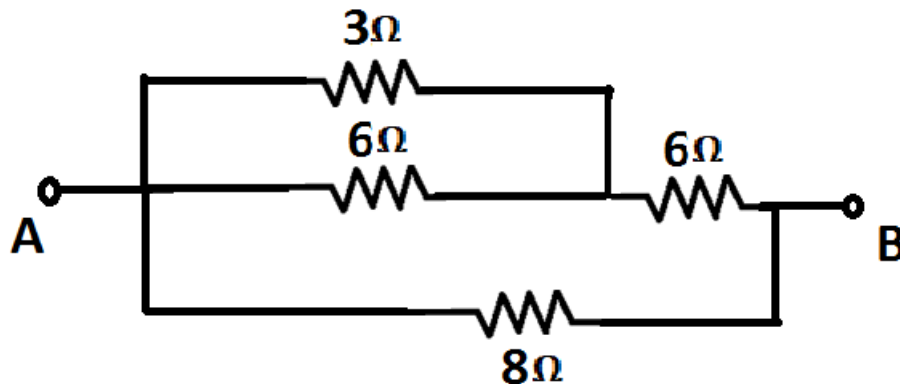

## Numerical Example – Finding Equivalent Resistance

Solution: (Continued..)

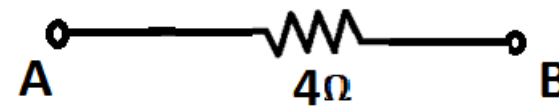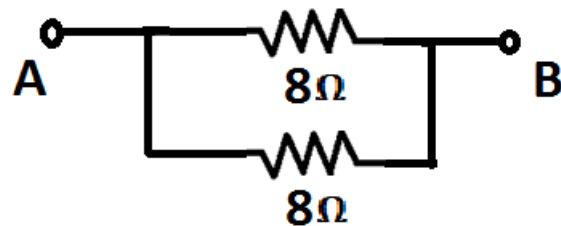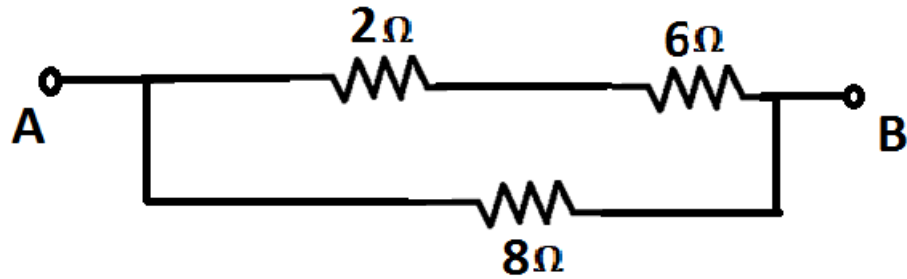

## Open Circuit

---


An Open Circuit has Infinite resistance.




Current through the Open Circuit is Zero.

Voltage across the Open Circuit can be any finite value.

## Open Circuit

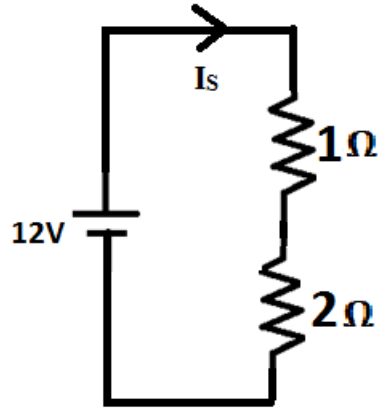

$$I_S = 4A$$

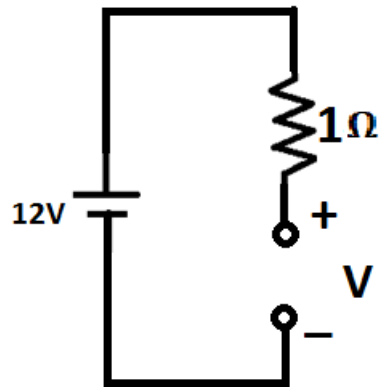


$$I_S = 0A$$
$$V = 12V$$

## Short Circuit

---

A Short Circuit has Zero resistance.

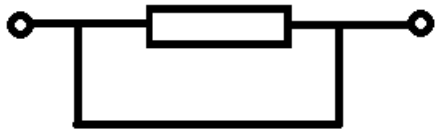


Voltage across a Short Circuit is Zero.


Current through the Short Circuit can be any finite value.

Current through a Dead Short Circuit is dangerously high.

## Short Circuit

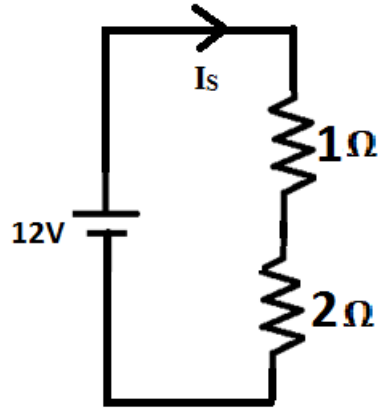

$$I_S = 4A$$

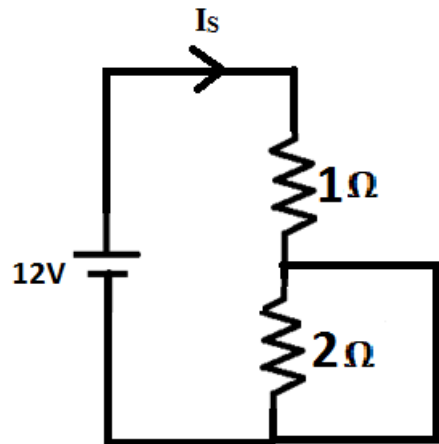

$$I_S = 12A$$

## Numerical Example – Open & Short Circuits


Find the equivalent resistance between X & Y if

i)  $R_a = \infty$  &  $R_b = \infty$

ii)  $R_a = 0$  &  $R_b = \infty$

iii)  $R_a = \infty$  &  $R_b = 0$

iv)  $R_a = 0$  &  $R_b = 0$

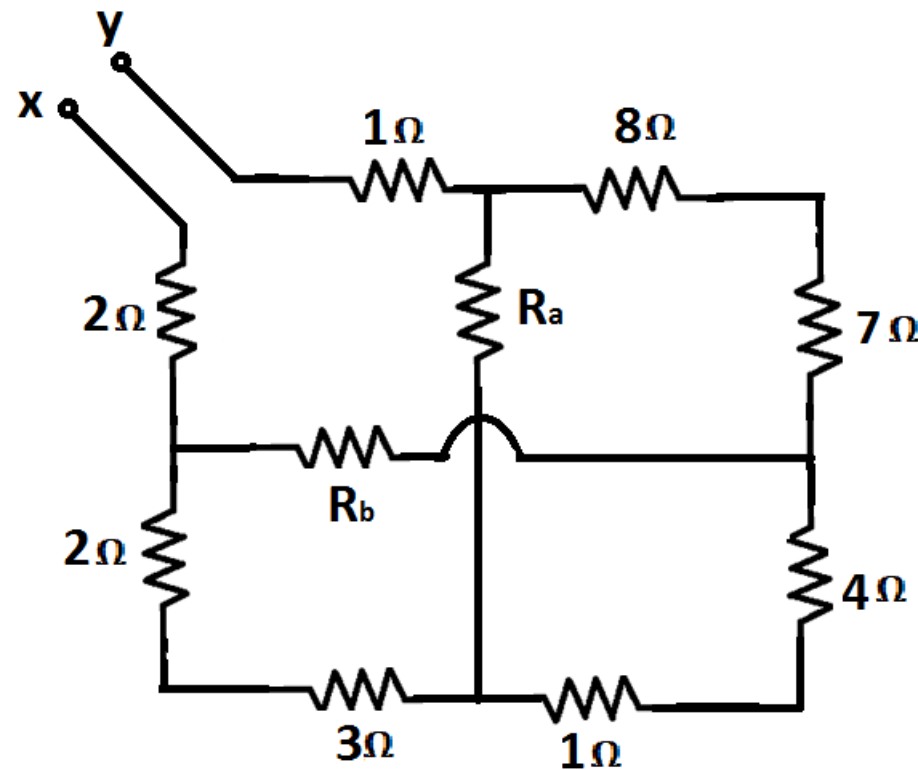




## Numerical Example – Open & Short Circuits

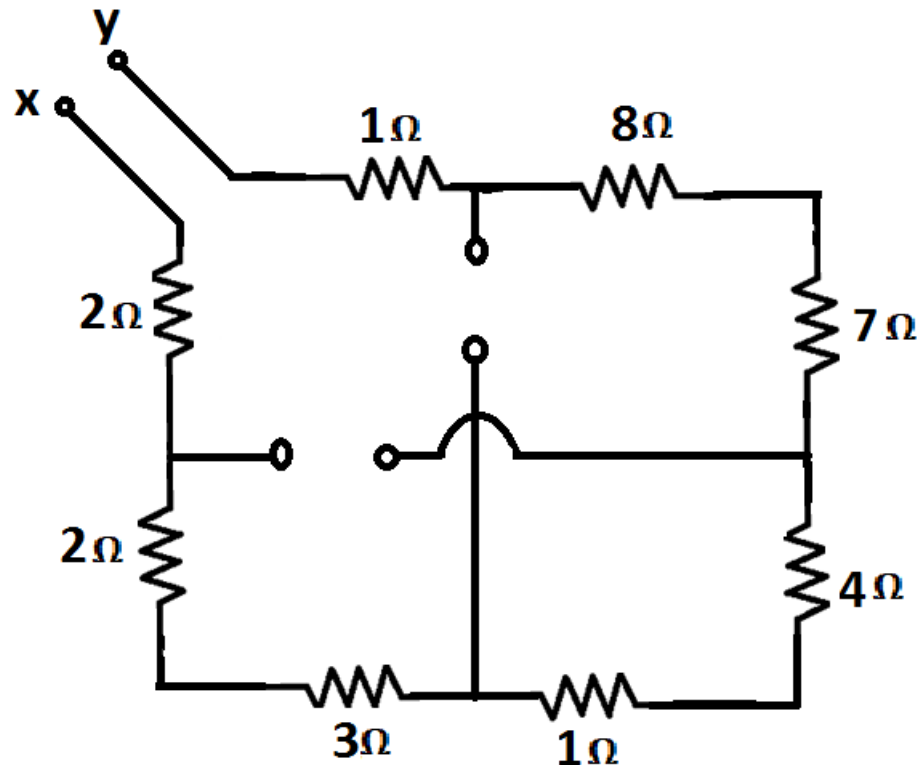**Solution:**

**Case i)**  $R_a = \infty$  &  $R_b = \infty$




All the resistors are  
in series.

Hence,  $R_{xy} = 28\Omega$

## Numerical Example – Open & Short Circuits

**Solution:**

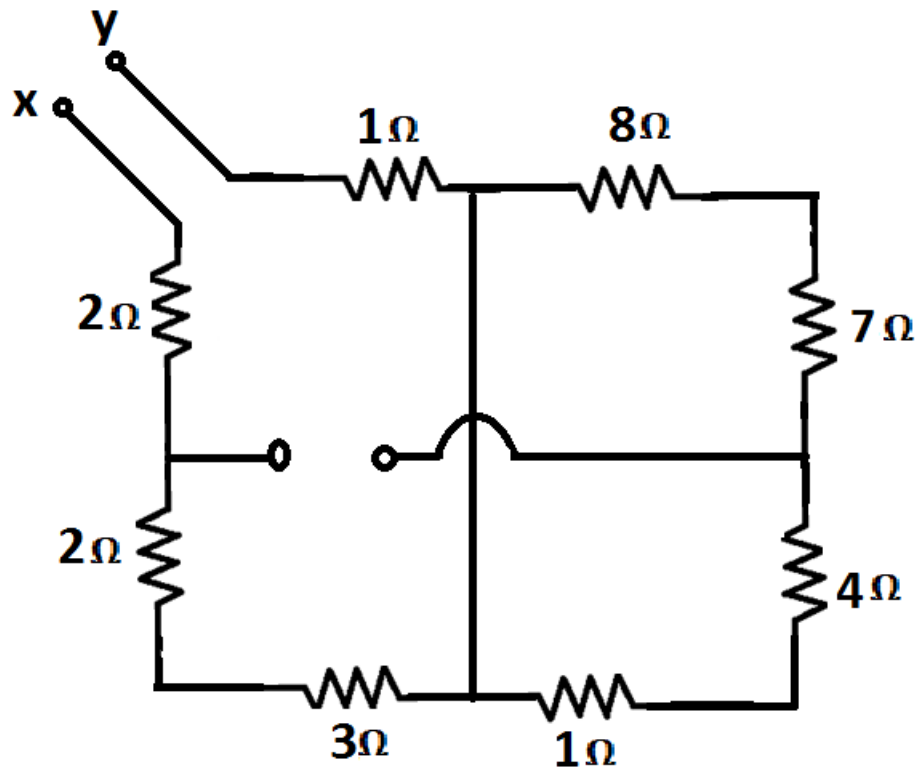**Case ii)  $R_a = 0$  &  $R_b = \infty$**





$$R_{XY} = 8\Omega$$

## Numerical Example – Open & Short Circuits

**Solution:**

**Case iv)  $R_a = 0$  &  $R_b = 0$**

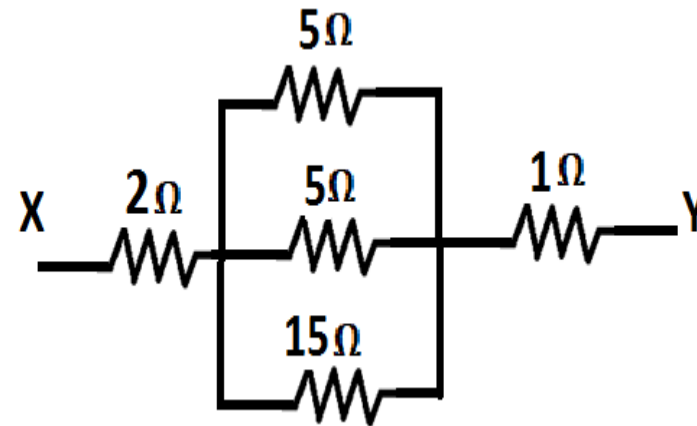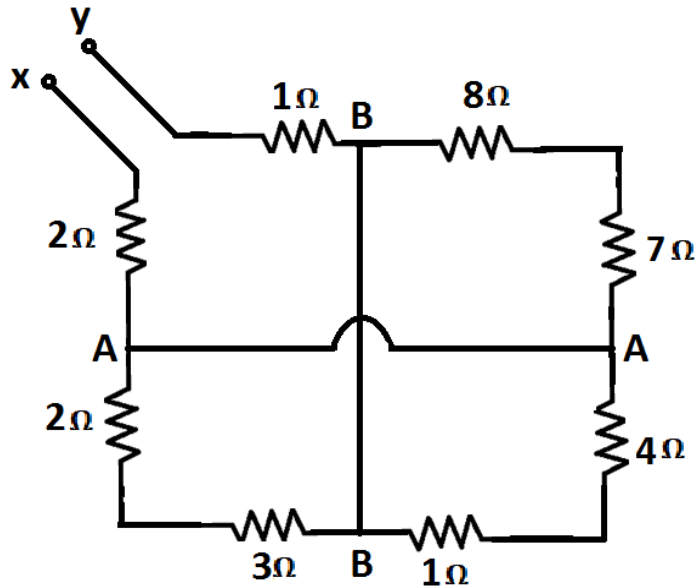

$$R_{XY} = 5.143\Omega$$

## Text Book & References

---

### Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11<sup>th</sup> Edition, Pearson Education, 2012.

### Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8<sup>th</sup> Edition, McGraw-Hill, 2012.



**THANK YOU**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**