



ELEMENTS OF ELECTRICAL ENGINEERING

UE24EE141B

Vadhiraj K P P

Department of Electrical & Electronics Engineering

ELEMENTS OF ELECTRICAL ENGINEERING

UE24EE141B

Lectures 17 & 18 -Numerical Examples on Thevenin's Theorem


Vadhiraj K P P

Department of Electrical & Electronics Engineering

Numerical Example 1

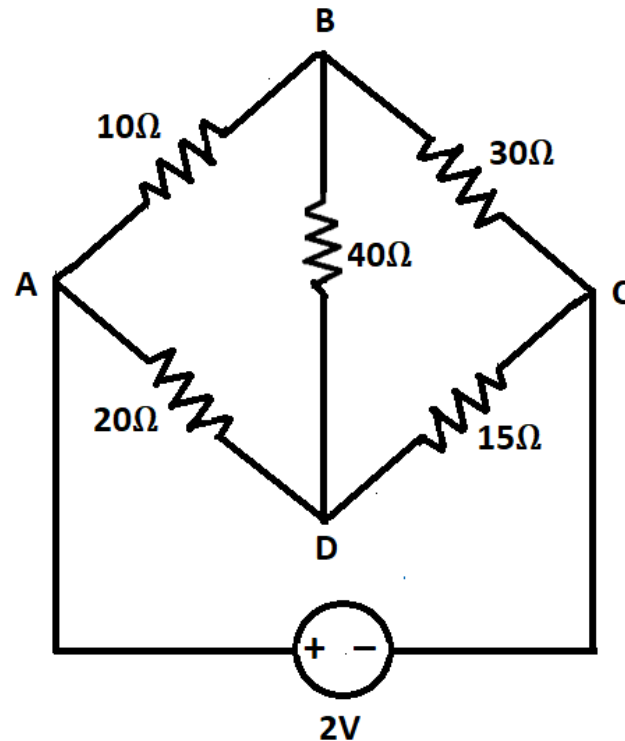Question:


Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown.



Numerical Example 1

Solution :

Finding V_{TH} :

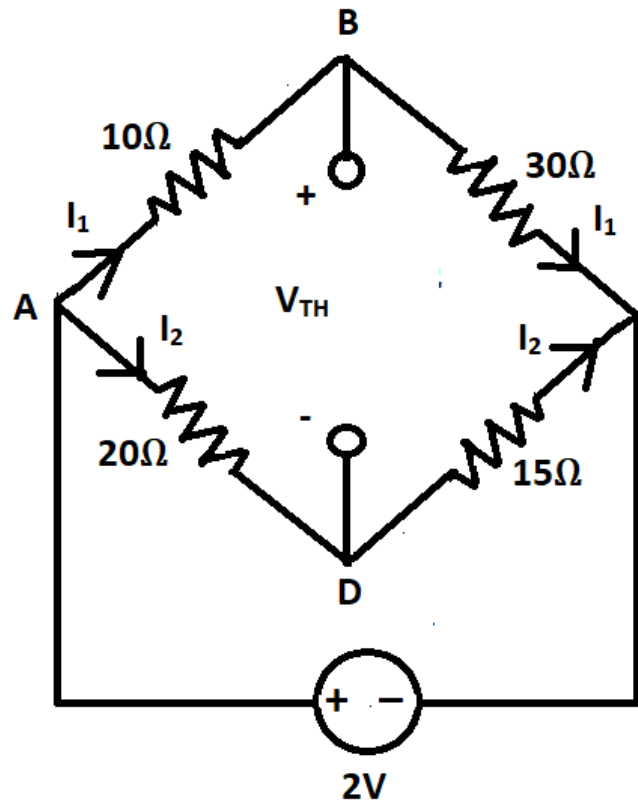

$$I_1 = \frac{2V}{40\Omega} = 0.05A ; I_2 = \frac{2V}{35\Omega} = 0.057A$$


By KVL (ABDA), $-10 \cdot I_1 - V_{TH} + 20 \cdot I_2 = 0$

$$V_{TH} = 0.64V$$


Numerical Example 1

Solution (Continued..) :

Finding R_{TH} :

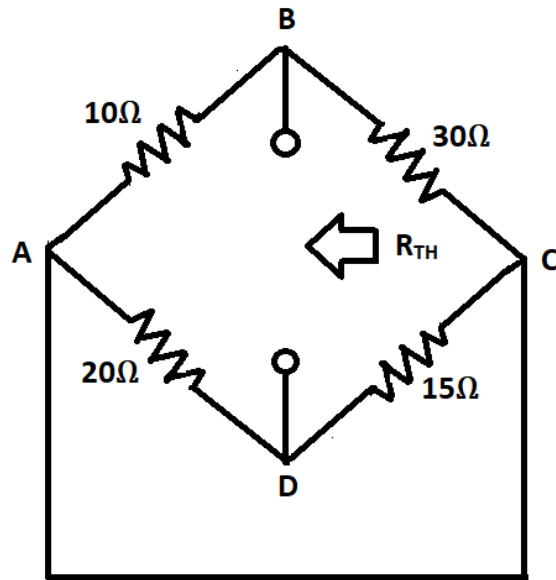

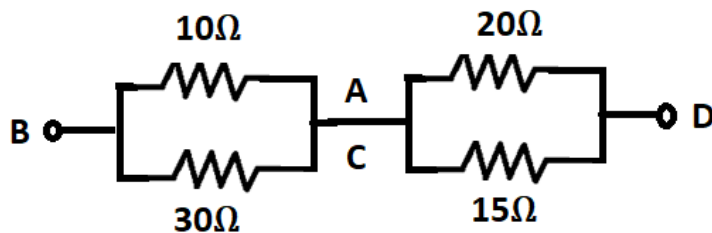
$$R_{TH} = (10\Omega \parallel 30\Omega) + (20\Omega \parallel 15\Omega) = 16.07\Omega$$



Numerical Example 1

Solution (Continued..) :

Thevenin's Equivalent Circuit:

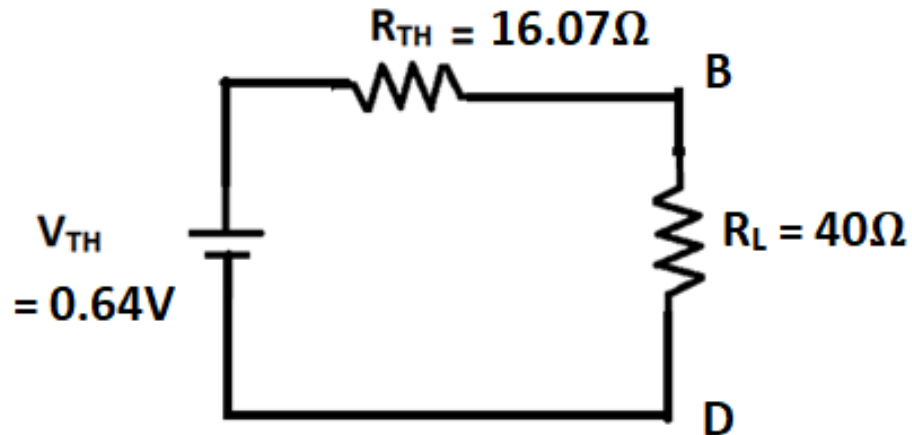


$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

Hence, current through the branch BD is 11.41mA and flows from terminal B to terminal D

Numerical Example 2

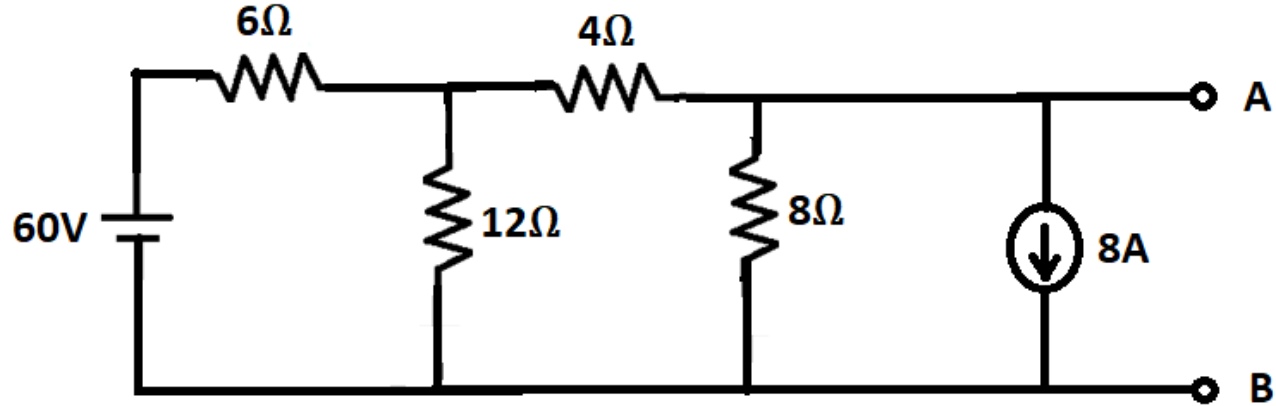Question:


Obtain the Thevenin's Equivalent across the terminals A & B for the network given.



Numerical Example 2

Solution :

Finding V_{TH} :

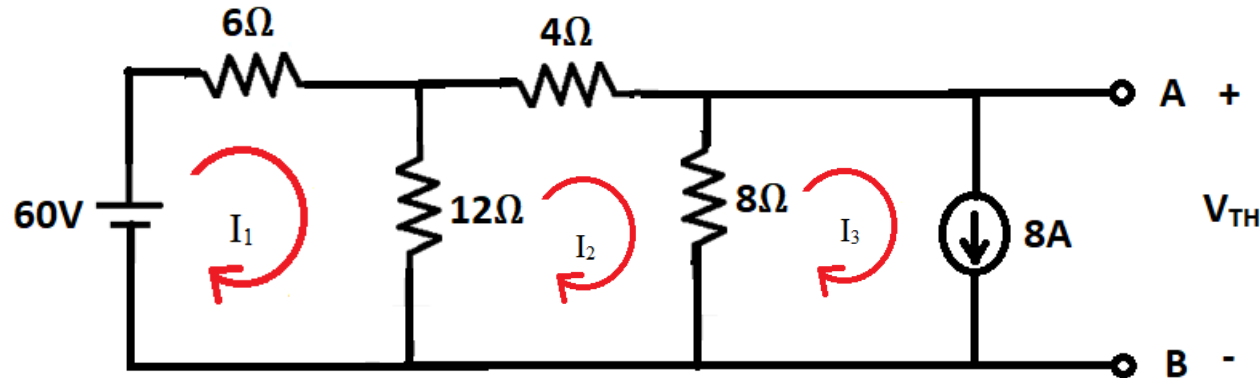

$$\text{KVL (Mesh 1)} : 18I_1 - 12I_2 - 0I_3 = 60 \quad \text{---- (1)}$$

$$\text{KVL (Mesh 2)} : -12I_1 + 24I_2 - 8I_3 = 0 \quad \text{---- (2)}$$

$$\text{Current Equation (Mesh 3)} : I_3 = 8 \quad \text{---- (3)}$$


Solving (1), (2) & (3), $I_1 = 7.66\text{A}$; $I_2 = 6.5\text{A}$

$$V_{TH} = (I_2 - I_3) * 8\Omega = -12\text{V}$$

Numerical Example 2

Solution (Continued..) :

Finding R_{TH} :

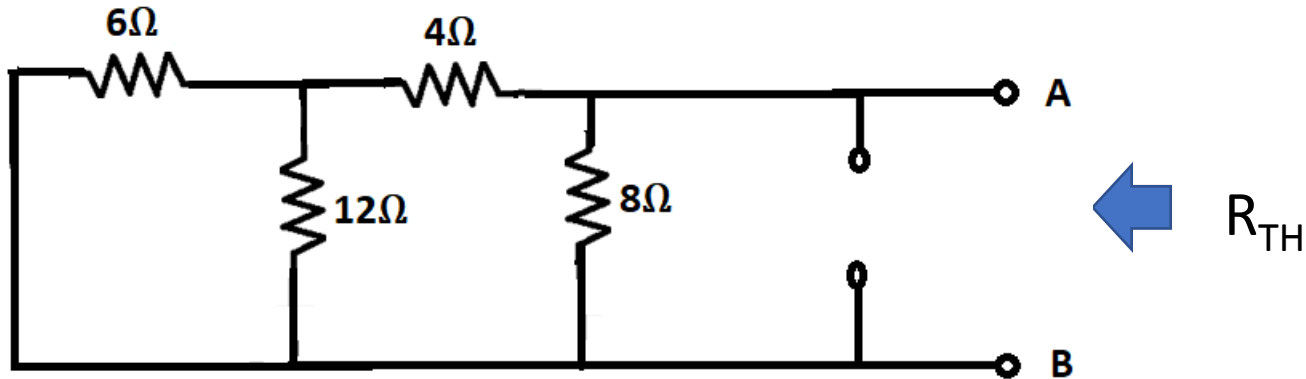


$$R_{TH} = \{(6\Omega \parallel 12\Omega) + 4\Omega\} \parallel 8\Omega = 4\Omega$$

Numerical Example 2

Solution (Continued..) :


Thevenin's Equivalent Circuit:

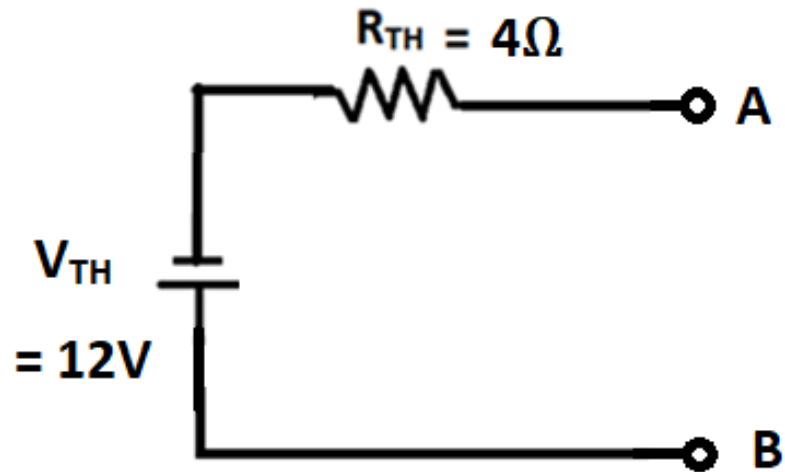


Assignment Question

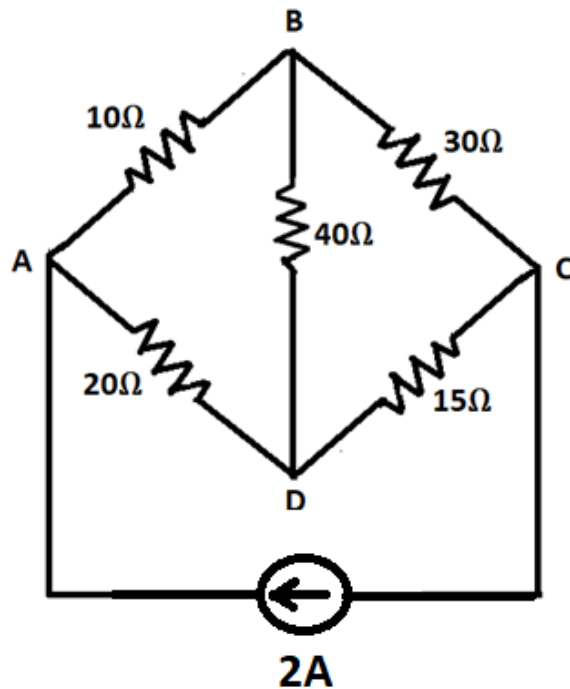Question:

Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown.




Numerical Example 2

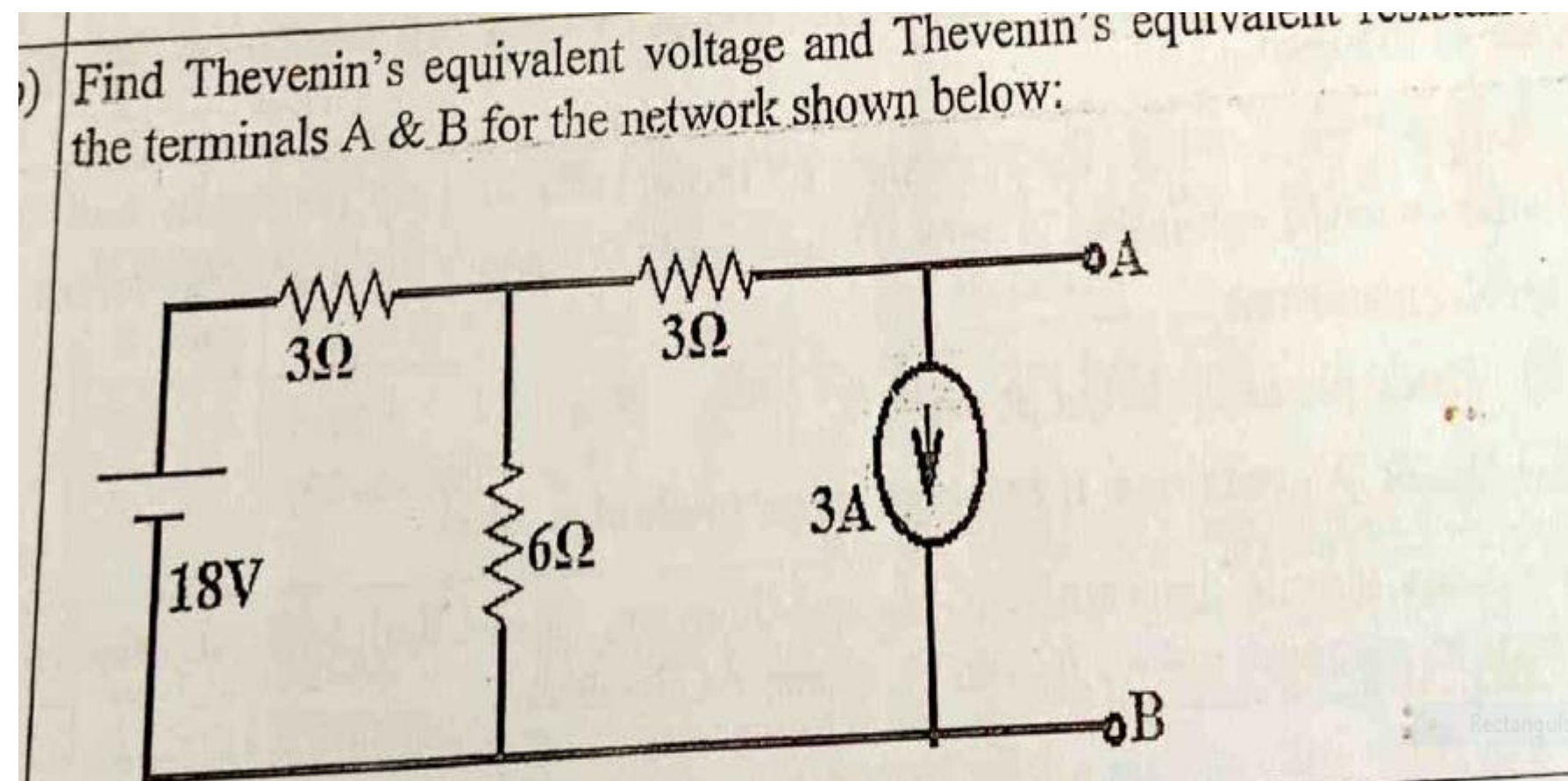


Numerical Example 2

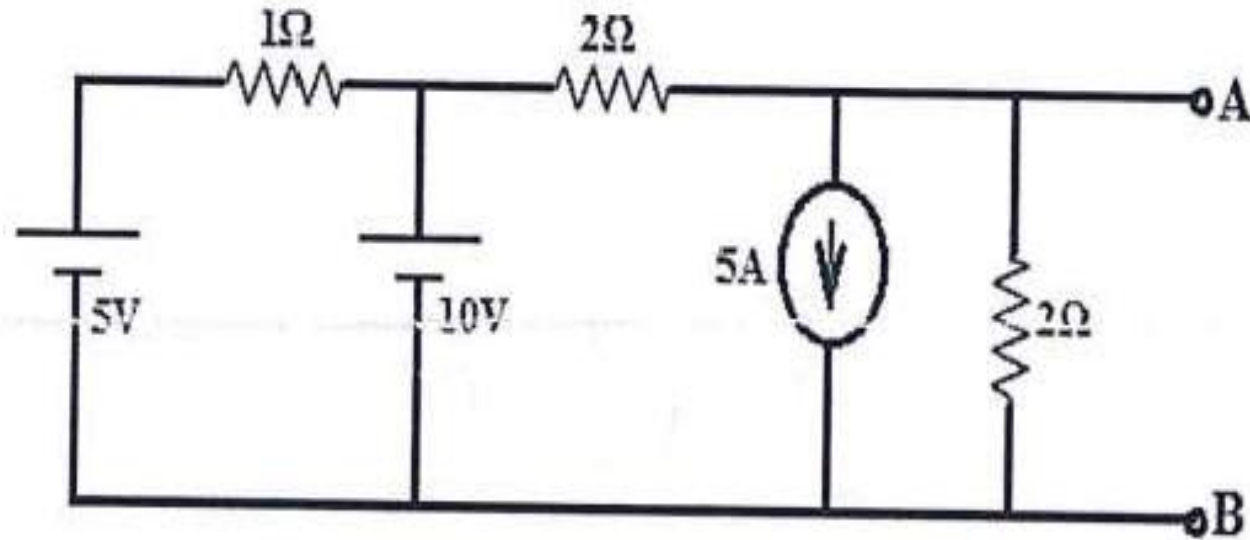b) Obtain the Thevenin's Equivalent across the terminals A & B in the network shown below:




Numerical Example 2

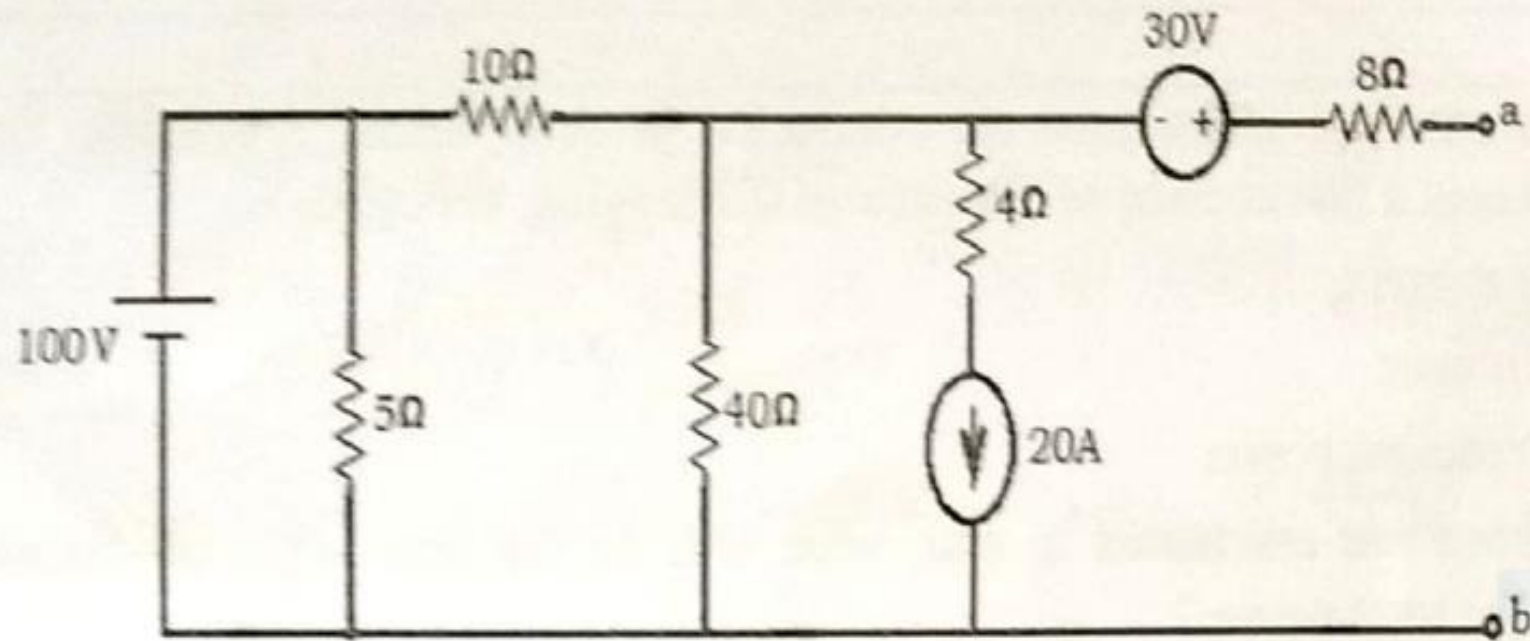
1. a) Find the Thevenin's equivalent across the terminals a & b in the circuit given.




Numerical Example 2

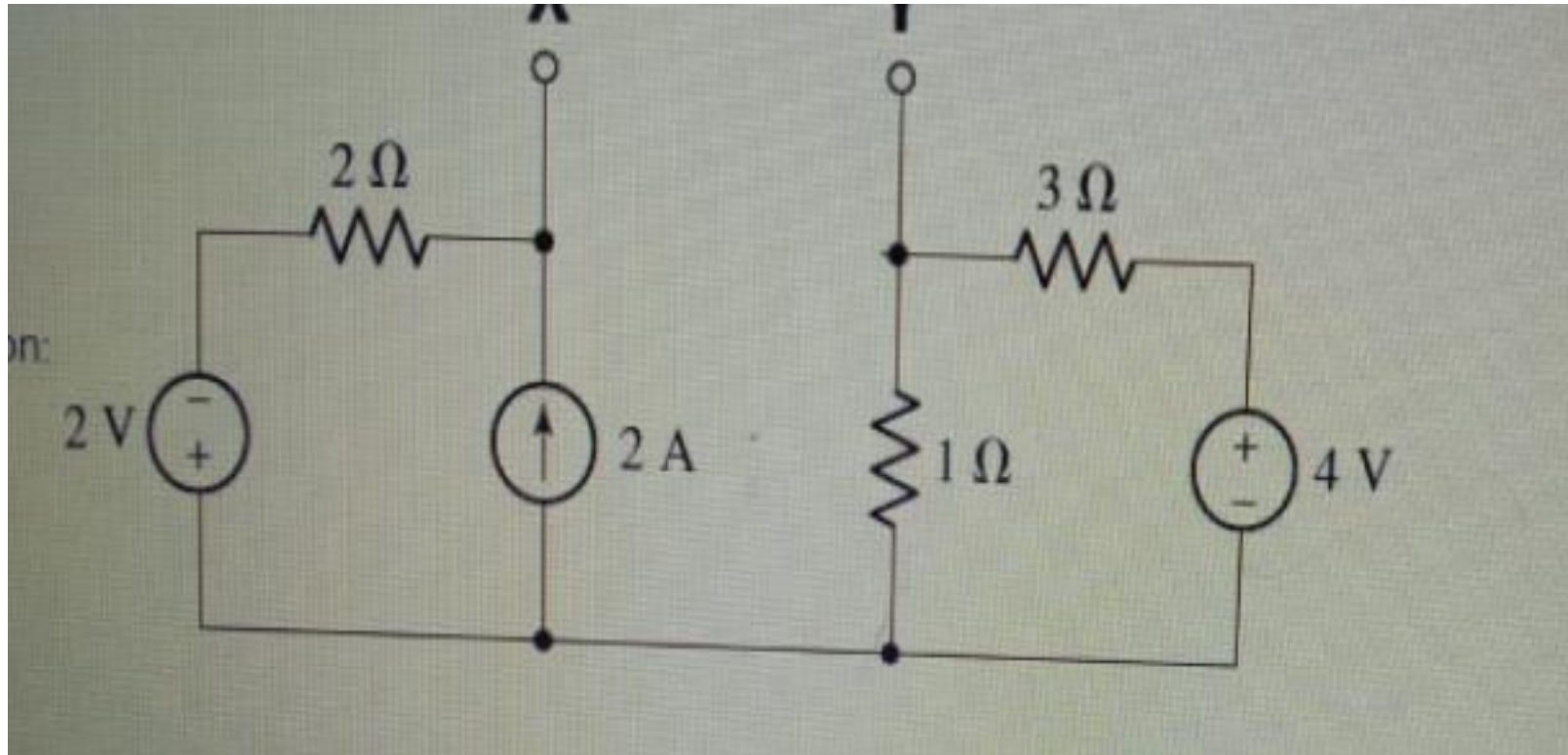

Numerical Example 2

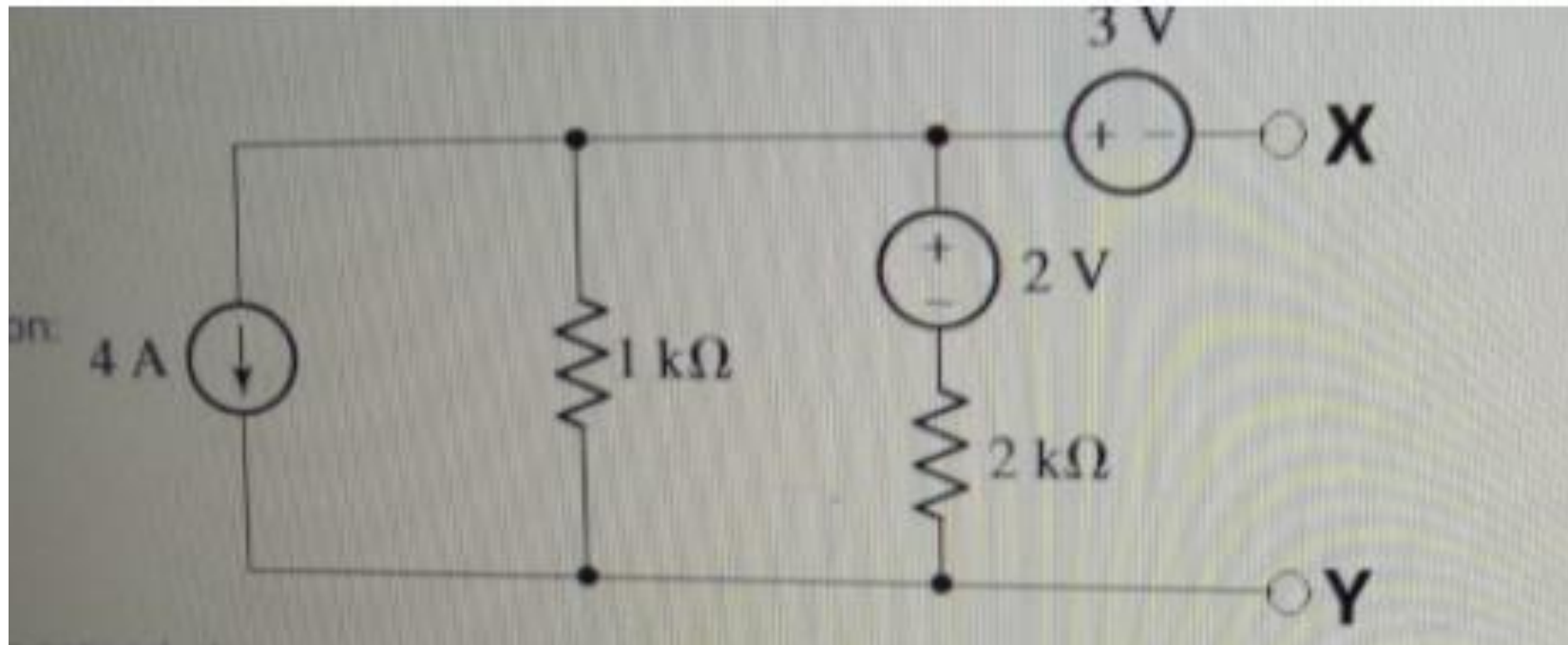

Numerical Example 2

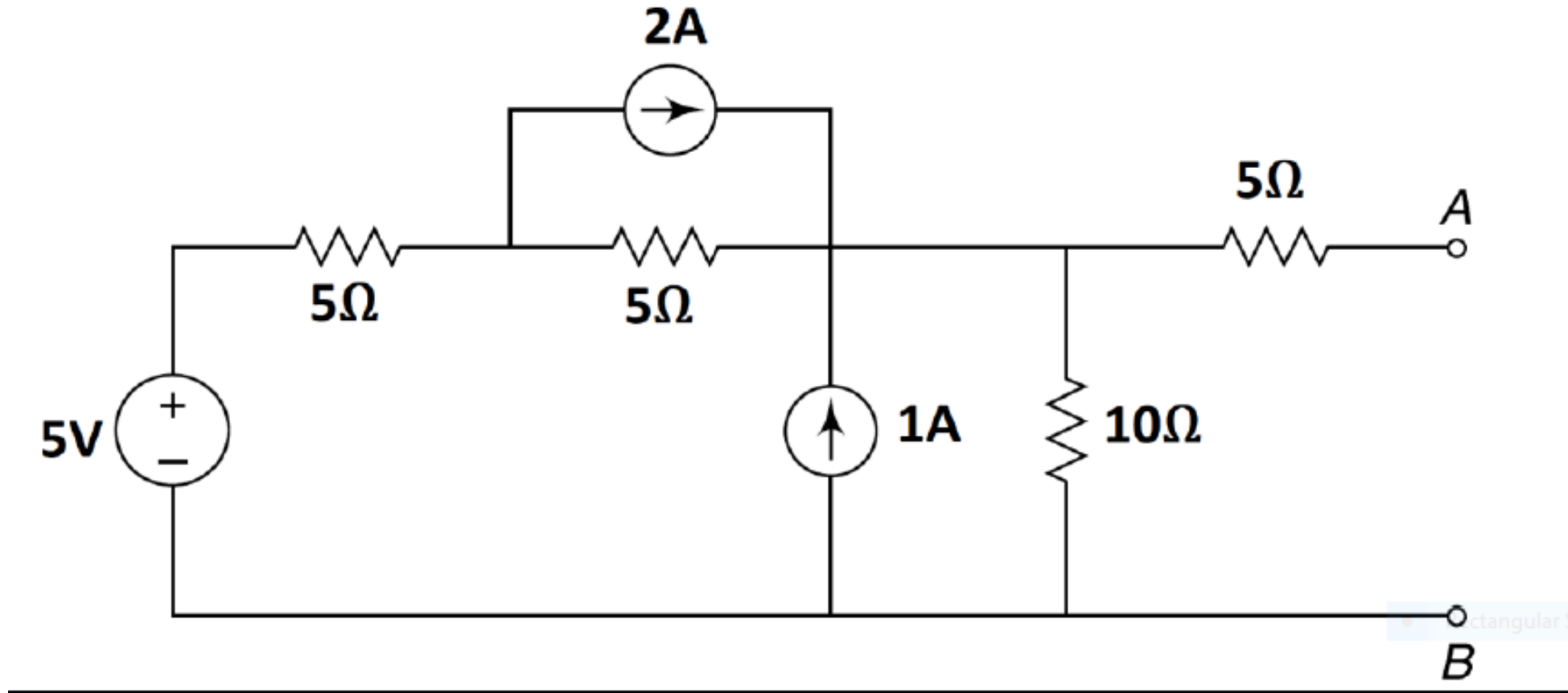

Text Book & References

Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11th Edition, Pearson Education, 2012.

Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8th Edition, McGraw-Hill, 2012.



THANK YOU

Vadhiraj K P P

Department of Electrical & Electronics Engineering

vadhirajkpp@pes.edu