



ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)

Vadhiraj K P P

Department of Electrical Engineering


ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)

Unit 2 – Lecture 23 - Analysis of Single-Phase AC circuits with R Load and L Load

Vadhiraj K P P

Department of Electrical & Electronics Engineering

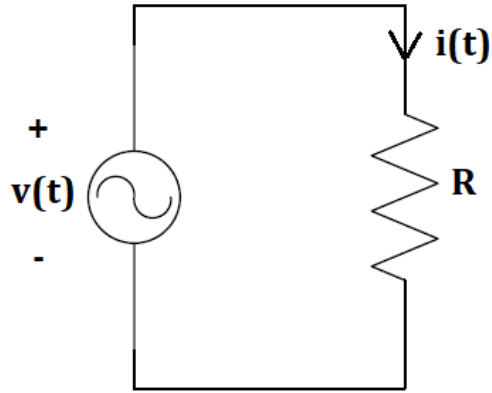Response of Resistive Load to Sinusoidal Supply



Let the supply voltage be $v(t) = V_m \sin(\omega t)$


where, V_m is the peak value of voltage

By Ohm's Law, $i(t) = \frac{v(t)}{R}$

Hence current will be of the form, $i(t) = I_m \sin(\omega t)$

where, $I_m = \frac{V_m}{R}$ is the peak value of current

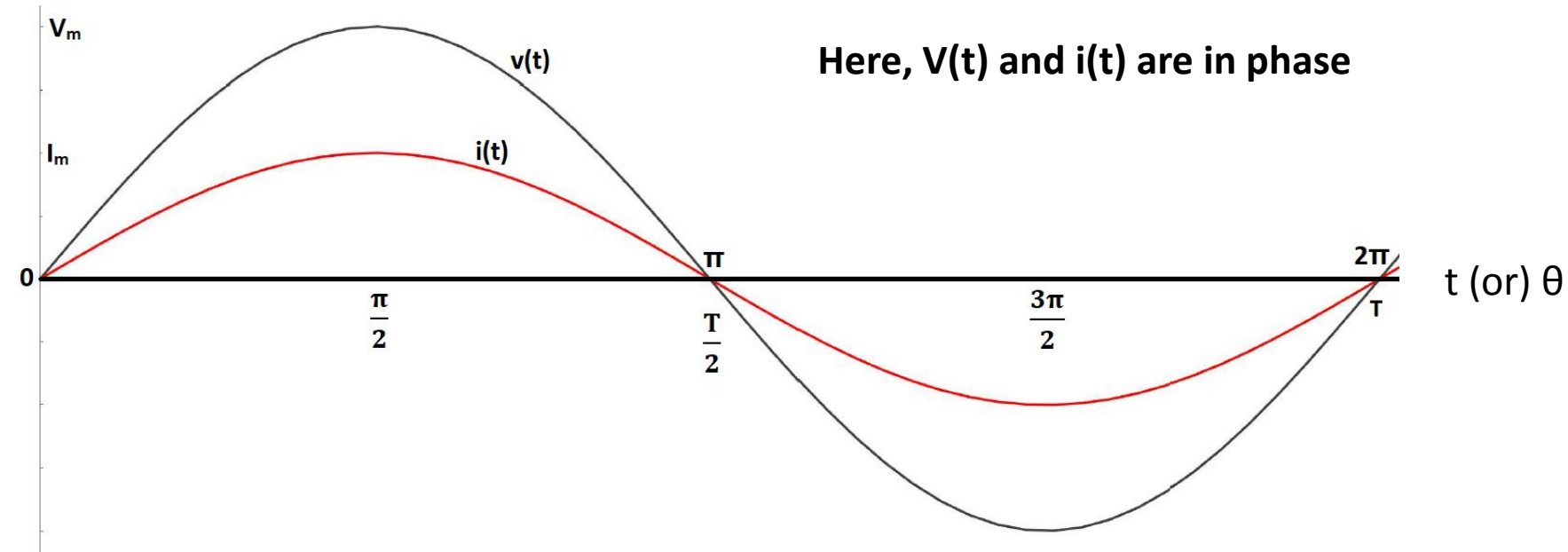Response of Resistive Load to Sinusoidal Supply



$$v(t) = V_m \sin(\omega t) \Rightarrow \bar{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$


$$i(t) = I_m \sin(\omega t) \Rightarrow \bar{I} = \frac{I_m}{\sqrt{2}} \angle 0^\circ$$

Phasor Diagram:



$$\text{Impedance, } Z = \frac{\bar{V}}{\bar{I}} = R \angle 0^\circ = R \, \Omega$$

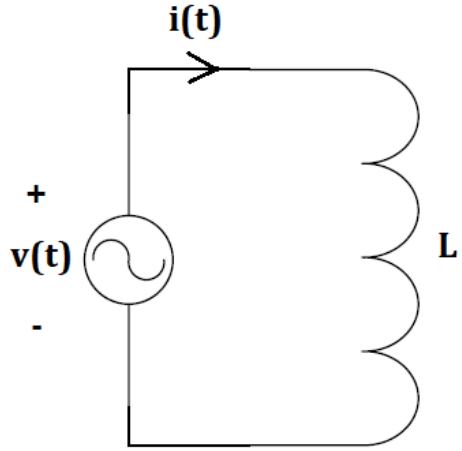Response of Pure Inductive Load to Sinusoidal Supply



Let the supply voltage be $v(t) = V_m \sin(\omega t)$


In a pure inductor, $i(t) = \frac{1}{L} \int v(t) dt$

$$= \frac{-V_m}{\omega L} \cos(\omega t)$$

$$= I_m \sin(\omega t - 90^\circ)$$

where, $I_m = \frac{V_m}{\omega L}$ is the peak value of current

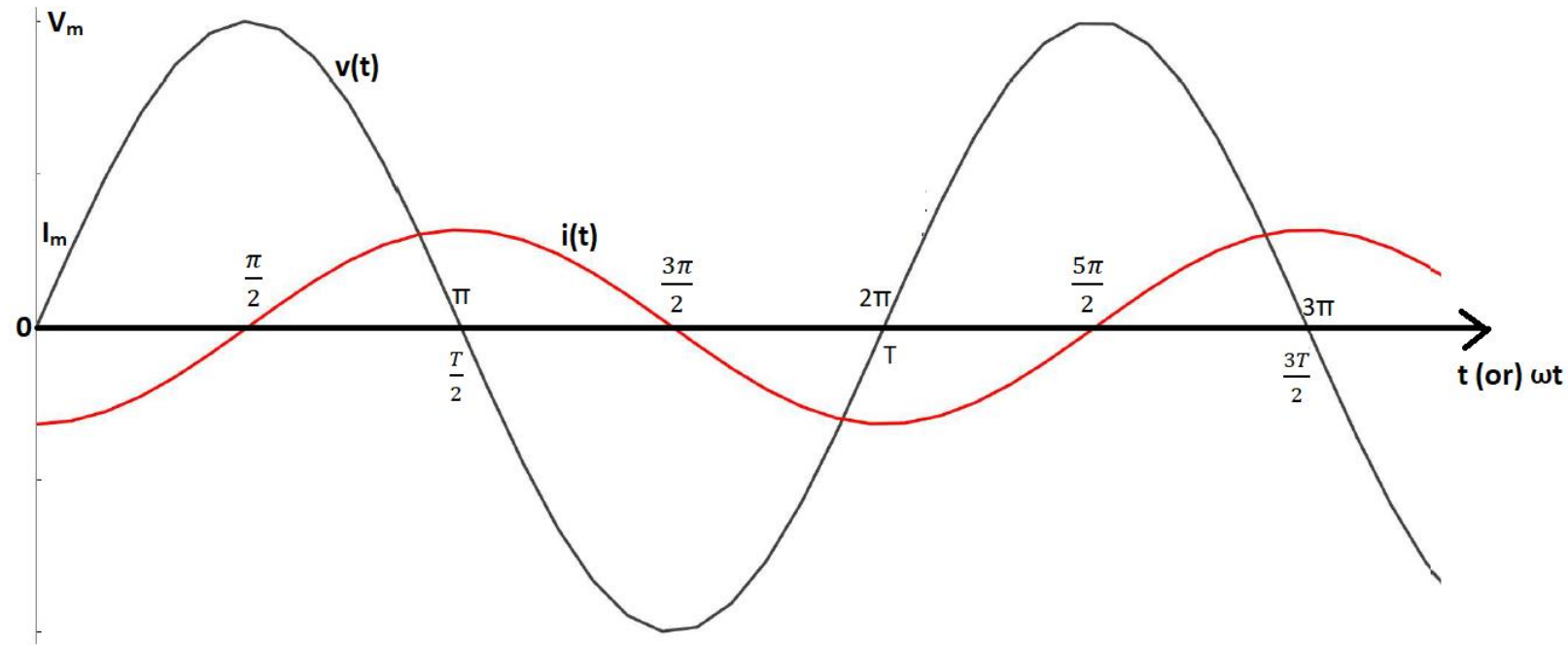Response of Pure Inductive Load to Sinusoidal Supply




In a pure inductor, current **lags** voltage by 90°

Response of Pure Inductive Load to Sinusoidal Supply

$$v(t) = V_m \sin(\omega t) \Rightarrow \bar{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$

$$i(t) = I_m \sin(\omega t - 90^\circ) \Rightarrow \bar{i} = \frac{I_m}{\sqrt{2}} \angle -90^\circ$$

Phasor Diagram:

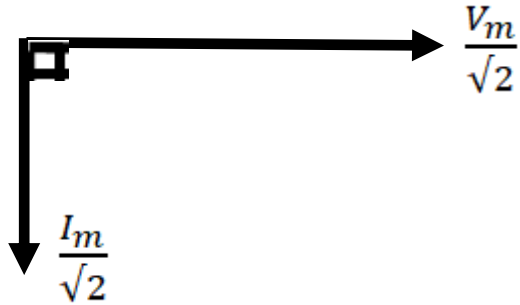

$$Z = \frac{\bar{V}}{\bar{i}} = \frac{\frac{V_m}{\sqrt{2}} \angle 0^\circ}{\frac{I_m}{\sqrt{2}} \angle -90^\circ} = \omega L \angle 90^\circ = jX_L \quad \Omega$$

Where, $X_L = \omega L$ is called '**Inductive Reactance**'

Text Book & References

Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11th Edition, Pearson Education, 2012.

Reference Books:

1. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
2. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8th Edition, McGraw-Hill, 2012.



THANK YOU

Vadhiraj K P P

Department of Electrical & Electronics Engineering

vadhirajkpp@pes.edu