



ELEMENTS OF ELECTRICAL ENGINEERING

UE24EE141B

Vadhiraj K P P

Department of Electrical & Electronics Engineering

ELEMENTS OF ELECTRICAL ENGINEERING

UE24EE141B


Lectures 6 & 7 - Practical Sources & Source Transformation; Numerical Examples

Vadhiraj K P P

Department of Electrical & Electronics Engineering


Practical Voltage Source

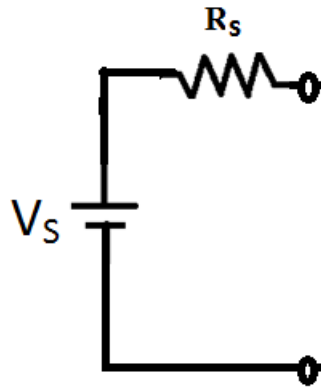- Its terminal voltage falls as load current increases.
- It is modelled as an ideal voltage source in series with internal resistance.




- Internal resistance is small, usually few $\text{m}\Omega$.
- Internal resistance of an ideal voltage source is Zero

Practical Voltage Source

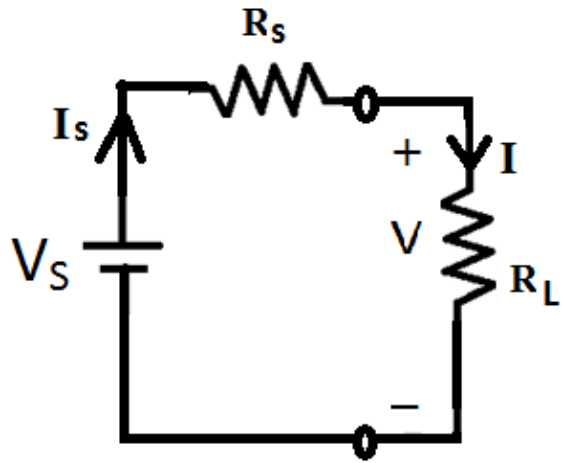


$$V = V_S - I * R_S$$

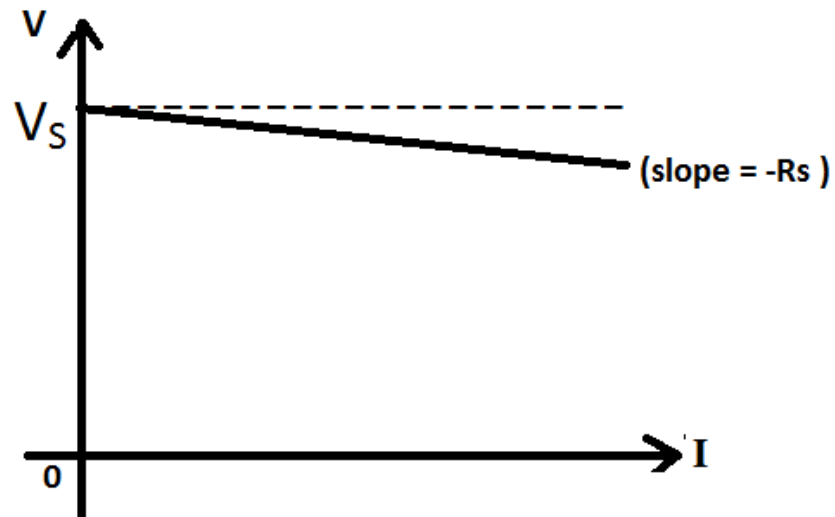


Practical Current Source

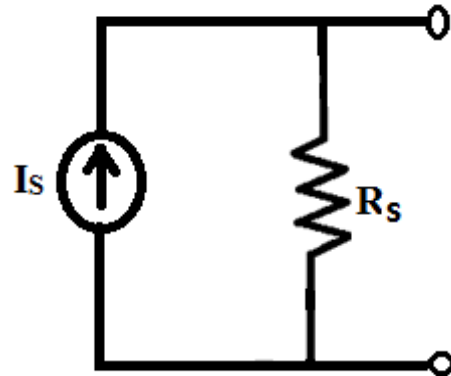- Its terminal current falls as load voltage increases.
- It is modelled as an ideal current source in parallel with internal resistance.




- Internal resistance is very high, usually few Mega Ohms
- Internal resistance of an ideal current source is Infinite

Practical Current Source

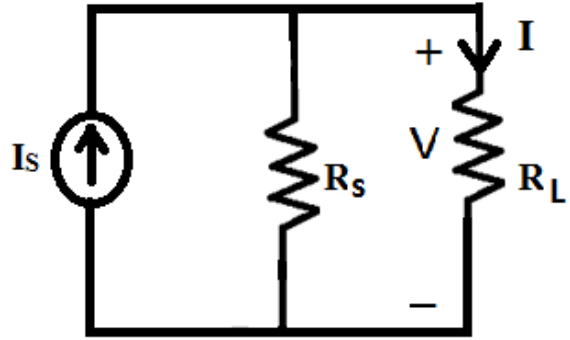
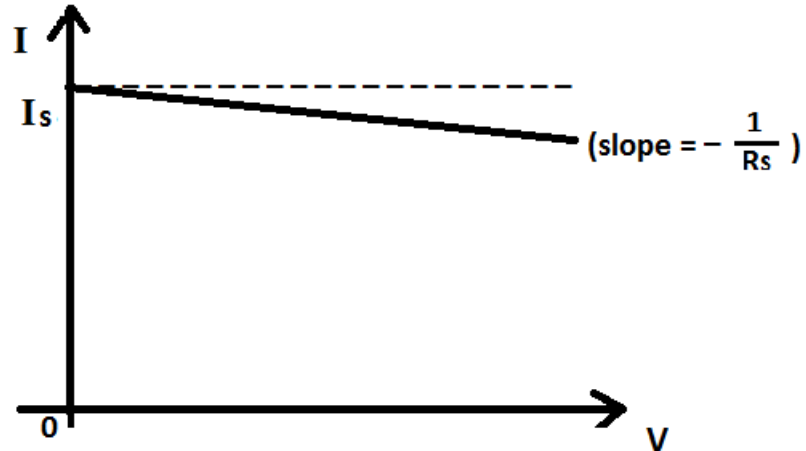
$$I = I_S - \left(\frac{V}{R_S} \right)$$




Numerical Example on Practical Sources

Question:

A battery of EMF 12V and internal resistance of 0.05Ω supplies power to a load resistance R_L . Determine the % change in load voltage as load resistance varies from 10Ω to 100Ω .

Solution:

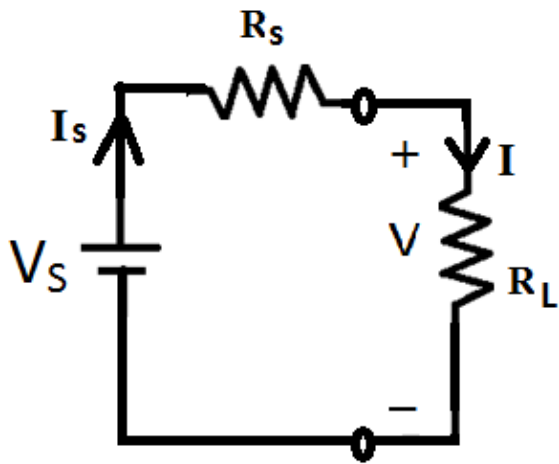


Case 1: $R_L = 10\Omega$

$$V = \frac{V_S * R_L}{(R_S + R_L)} = 11.94V$$

(By Voltage Division)

Numerical Example on Practical Sources

Solution (Continued..):

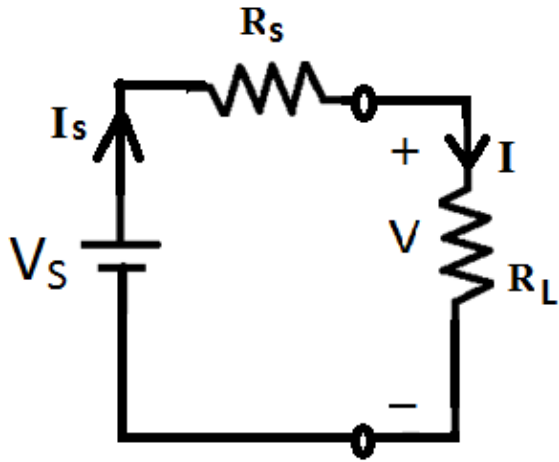

Case 2: $R_L = 100\Omega$

$$V = \frac{V_S * R_L}{(R_S + R_L)} = 11.99V$$

% Change in the load voltage =


$$\frac{(11.99 - 11.94)}{11.94} * 100 = 0.42\%$$

Numerical Example on Practical Sources

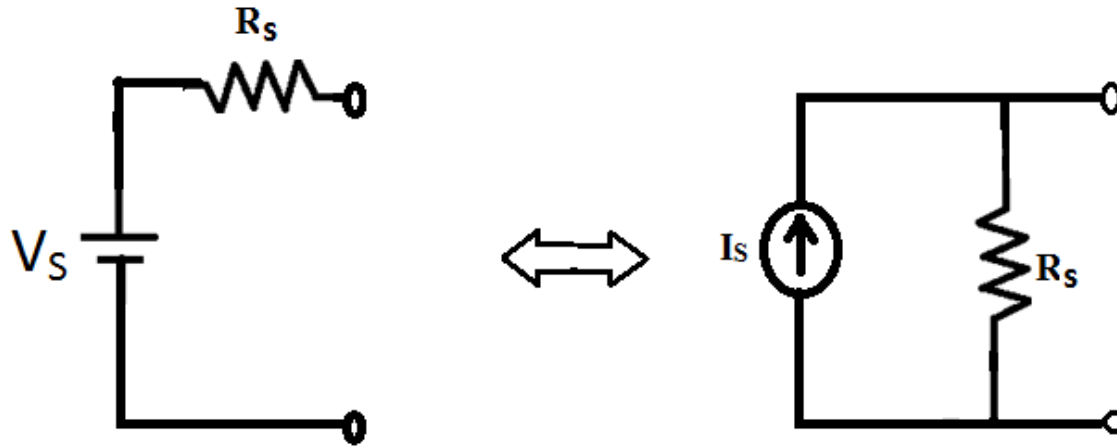Q2. Two batteries A and B are connected in parallel and a load of 10Ω is connected across them. Battery A has an emf of 9V and internal resistance of 0.5Ω and B has an emf of 12V and internal resistance of 1Ω . Determine i) the magnitude and the direction of current flowing through load resistance, ii) current supplied by each battery and iii) potential difference across the load resistance.

Source Transformation


A Practical Voltage Source can be transformed to a Practical Current Source & Vice versa.




Two Sources are equivalent if they supply same terminal voltage and current when loaded with same load resistance.

Source Transformation

Case 1: Open Circuit Condition

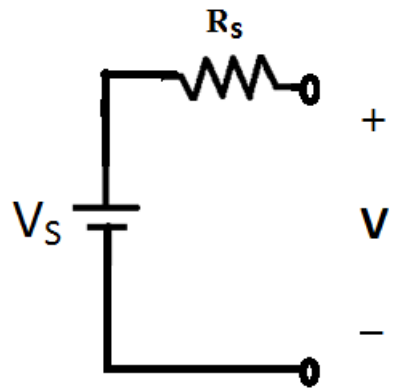

$$V = V_S$$

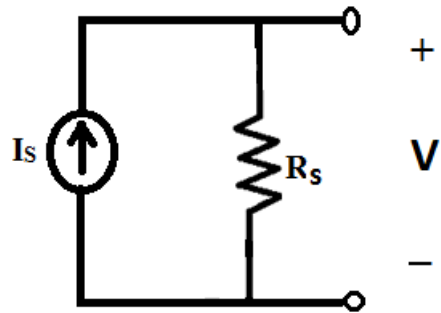


$$V = I_S * R_S$$


$$\text{Hence, } V_S = I_S * R_S$$

Source Transformation

Case 2: Short Circuit Condition

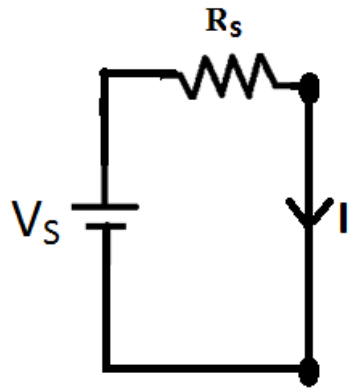

$$I = \frac{V_S}{R_S}$$

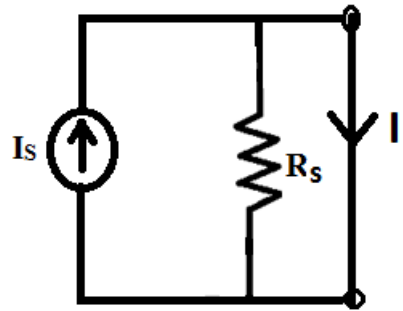


$$I = I_S$$

$$\text{Hence, } V_S = I_S * R_S$$


Numerical Example on Source Transformation

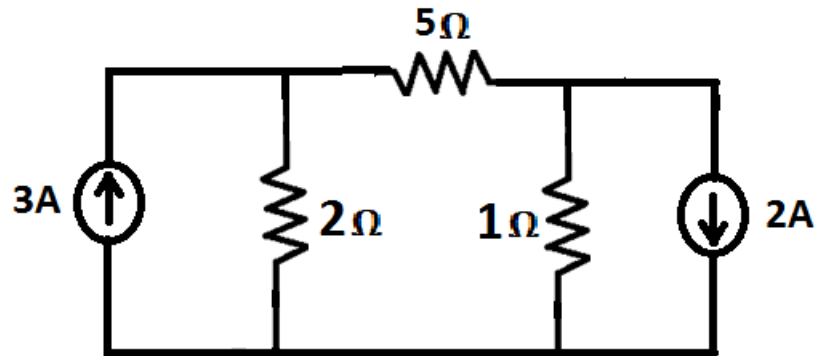Question:

Find the current through 5Ω resistor in the network shown:



Solution:


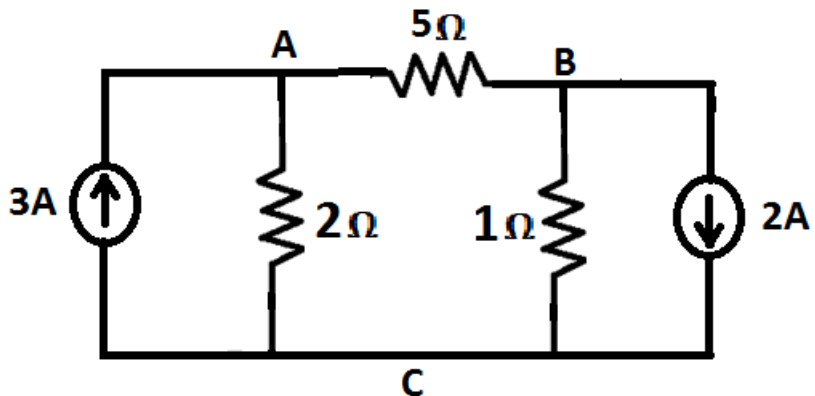


Replace $3A$ current source & 2Ω resistance with equivalent practical voltage source.

Repeat the same for $2A$ current source & 1Ω resistance.

Numerical Example on Practical Sources

Solution (Continued..):

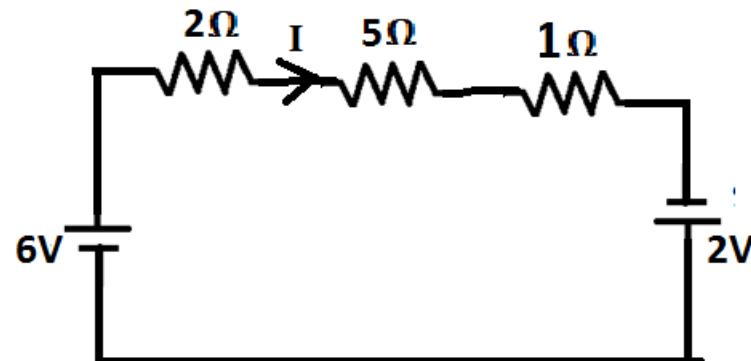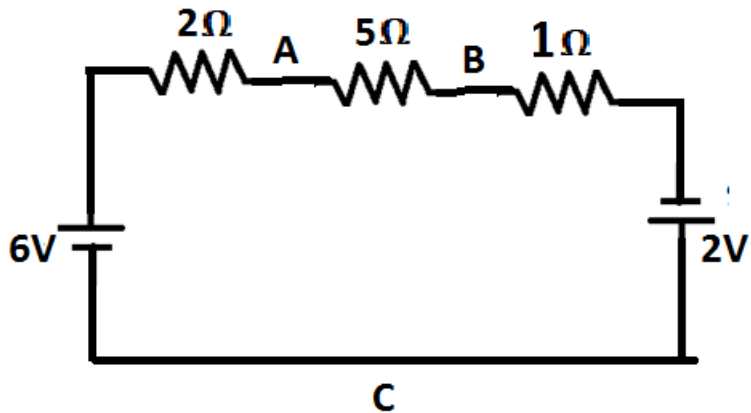

By applying KVL

$$+6 - 2I - 5I - I + 2 = 0$$

$$I = 1A$$

Source Transformation

Q3. A current of 20A flows through two ammeters A and B joined in series. Across A the potential difference is 0.2V and across B it is 0.3V. Find how the same current will divide between A and B when they are joined in parallel.

Text Book & References

Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11th Edition, Pearson Education, 2012.

Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8th Edition, McGraw-Hill, 2012.



THANK YOU

Vadhiraj K P P

Department of Electrical & Electronics Engineering

vadhirajkpp@pes.edu