



ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)

Vadhiraj K P P

Department of Electrical Engineering


ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)

Unit 2 – Lectures 32 & 33 - Analysis of Parallel RLC circuit ; Numerical examples

Vadhiraj K P P

Department of Electrical & Electronics Engineering

Parallel RLC Circuit

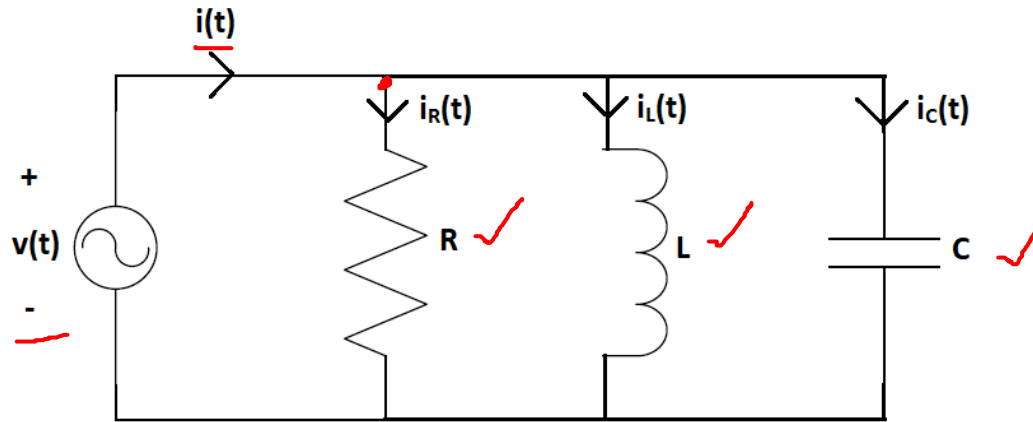

By KCL, $i(t) = i_R(t) + i_L(t) + i_C(t)$

In Phasor form, $\bar{i} = \bar{i}_R + \bar{i}_L + \bar{i}_C$

$$\bar{i}_R = \bar{V} * G \quad \bar{i}_L = \bar{V} * (-jB_L) \quad \bar{i}_C = \bar{V} * (jB_C)$$

$$\bar{i} = \bar{V} * (G - jB_L + jB_C)$$

$$\textcircled{Y_T} = \frac{\bar{i}}{\bar{V}} = (G - jB_L + jB_C) = \sqrt{G^2 + (B_C - B_L)^2} \angle \tan^{-1}\left(\frac{B_C - B_L}{G}\right)$$

$$\phi = -\tan^{-1}\left(\frac{B_C - B_L}{G}\right)$$


Case 1: $B_L > B_C$

If $B_L > B_C$ then $VB_L > VB_C$

i.e., $|\bar{I}_L| > |\bar{I}_C|$

The circuit behaves effectively as inductive circuit i.e., parallel RL type.

Phasor Diagram:

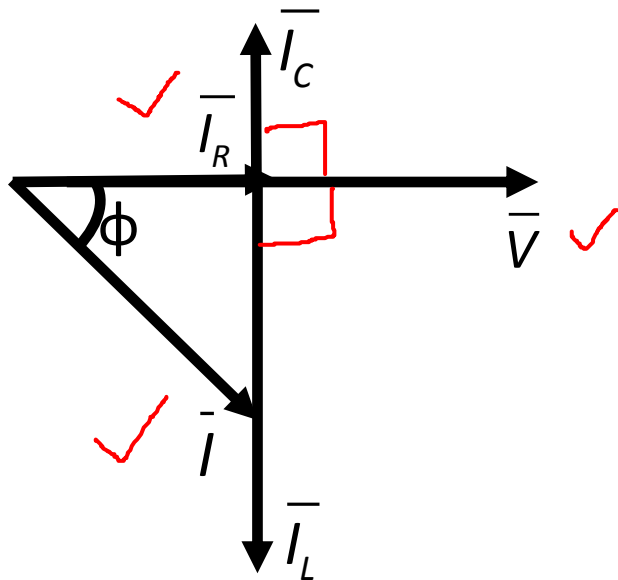

$$\phi = \tan^{-1} \left(\frac{B_C - B_L}{G} \right)$$


$\phi = \text{positive}$

If $B_C > B_L$ then $VB_C > VB_L$

i.e., $|\bar{I}_C| > |\bar{I}_L|$

The circuit behaves effectively as a capacitive circuit i.e., parallel RC type.

Phasor Diagram:

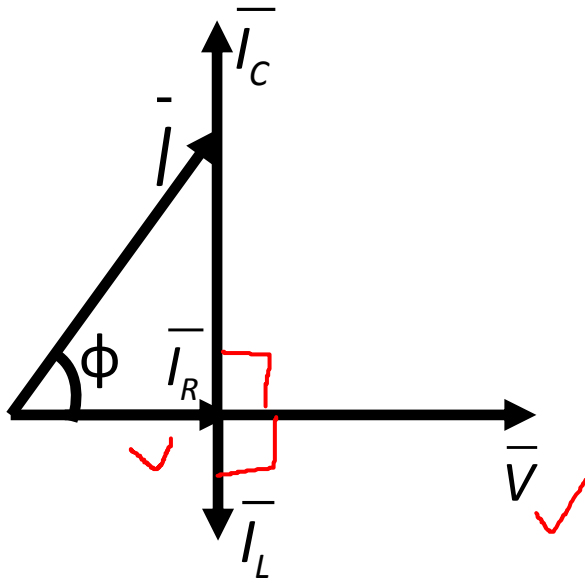

$$\phi = -\tan^{-1}\left(\frac{B_C - B_L}{G}\right)$$


Note: ϕ will be negative in this case since $B_L < B_C$

Case 3: $B_L = B_C$

If $B_L = B_C$ then $VB_L = VB_C$ i.e., $|\bar{I}_L| = |\bar{I}_C|$

The circuit behaves effectively as a purely resistive circuit. This case is called '**Parallel Resonance**' case.

Phasor Diagram:

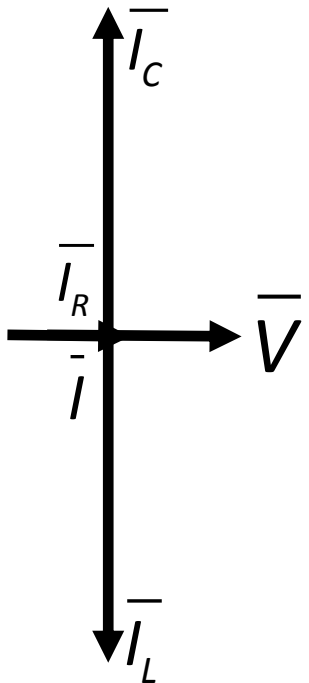

$$\bar{I} = \bar{I}_R$$

$$Y = G$$

$$\phi = 0^\circ$$

Numerical Example


Question:

Three circuit elements $R=2.5\Omega$, $X_L=4\Omega$ and $X_C=10\Omega$ are connected in parallel, the reactances being at 50Hz.

- Determine the admittance of each element and hence obtain the input admittance.
- If this circuit is connected across a 10V, 50Hz AC source, determine the current in each branch and the total input current.

Numerical Example

Solution:

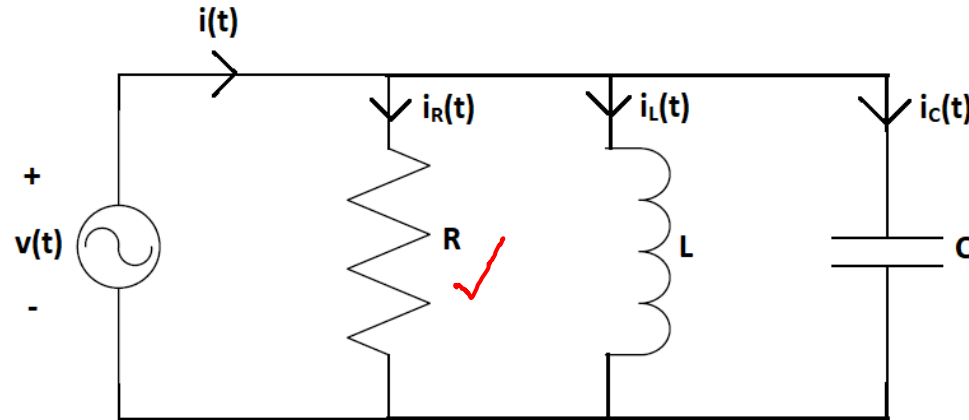

i) Admittance of branch1, $Y_1 = \frac{1}{Z_1} = \frac{1}{R} = G = \underline{0.4S}$


Admittance of branch2, $Y_2 = \frac{1}{Z_2} = \frac{1}{jX_L} = -jB_L = \underline{-j0.25S}$

Admittance of branch3, $Y_3 = \frac{1}{Z_3} = \frac{1}{-jX_C} = jB_C = \underline{j0.1S}$

Input Admittance $Y_{in} = \underline{Y_T} = Y_1 + Y_2 + Y_3 = (0.4 - j0.15)S$

Numerical Example

Solution (Continued..) :

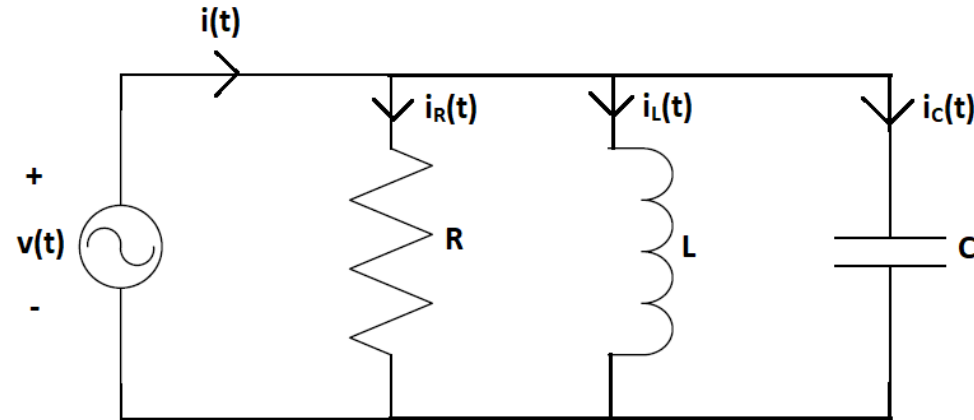

ii) Taking supply voltage as reference, $\bar{V} = 10\angle 0^\circ \text{V}$

current in branch 1, $\bar{I}_R = \frac{\bar{V}}{Z_1} = \bar{V}Y_1 = 10\angle 0^\circ * 0.4 = 4\angle 0^\circ \text{A}$

current in branch 2, $\bar{I}_L = \bar{V}Y_2 = 10\angle 0^\circ * (-j0.25) = 2.5\angle -90^\circ \text{A}$

current in branch 3, $\bar{I}_C = \bar{V}Y_3 = 1\angle 90^\circ \text{A}$

Input current, $\bar{I}_S = \bar{I}_R + \bar{I}_L + \bar{I}_C = 4.27\angle -20.55^\circ \text{A}$

Numerical Example

Q10. The admittance of a circuit is $(0.05-j0.08)\text{S}$. Find the values of the resistance and inductive reactance of the circuit if they are a) in parallel b) in series.

Rectangular Snip

Impedance of a two-element parallel AC network is $(6+j8)\ \Omega$. Determine the elements and their values if the supply frequency is 50Hz.

4M

ask this
answer to
atharva

Text Book & References

Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11th Edition, Pearson Education, 2012.

Reference Books:

1. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
2. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8th Edition, McGraw-Hill, 2012.



THANK YOU

Vadhiraj K P P

Department of Electrical & Electronics Engineering

vadhirajkpp@pes.edu