



ELEMENTS OF ELECTRICAL ENGINEERING

UE24EE141B

Vadhiraj K P P

Department of Electrical & Electronics Engineering

ELEMENTS OF ELECTRICAL ENGINEERING

UE24EE141B


Lecture 11 - Mesh Analysis

Vadhiraj K P P

Department of Electrical & Electronics Engineering

Concepts of Loop and Mesh

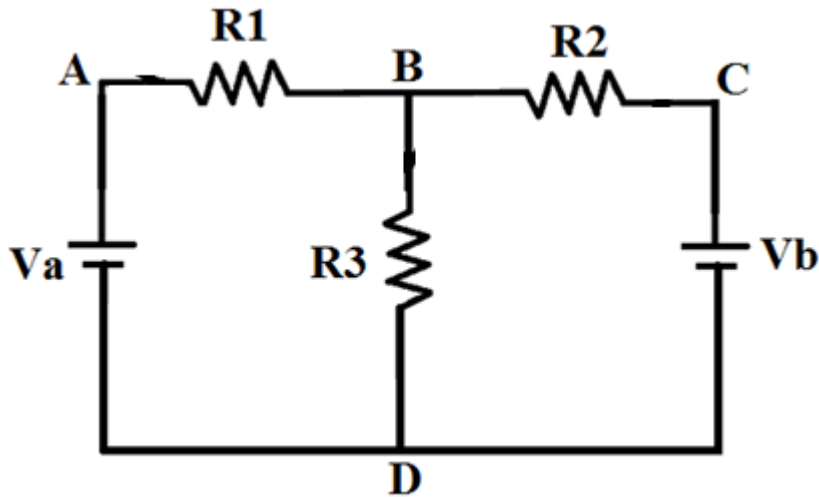- A Loop is a closed path with current flow in every element in that path.
- A mesh is a fundamental loop. It doesn't have smaller loops within itself.



Loops:

A-B-D-A
B-C-D-B
A-B-C-D-A


Meshes:

A-B-D-A
B-C-D-B

Steps to apply Mesh Analysis

Step 1: Identify the number of meshes in the network.

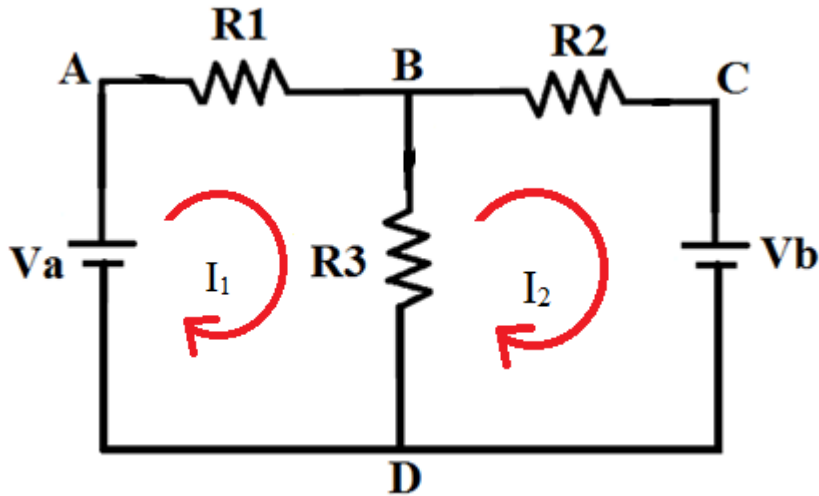Step 2: Assign one mesh current in each mesh preferably in the same direction.




Step 3: Write KVL in every mesh.

Step 4: Solve simultaneous equations to obtain Mesh currents.

Mesh Analysis – Numerical Example

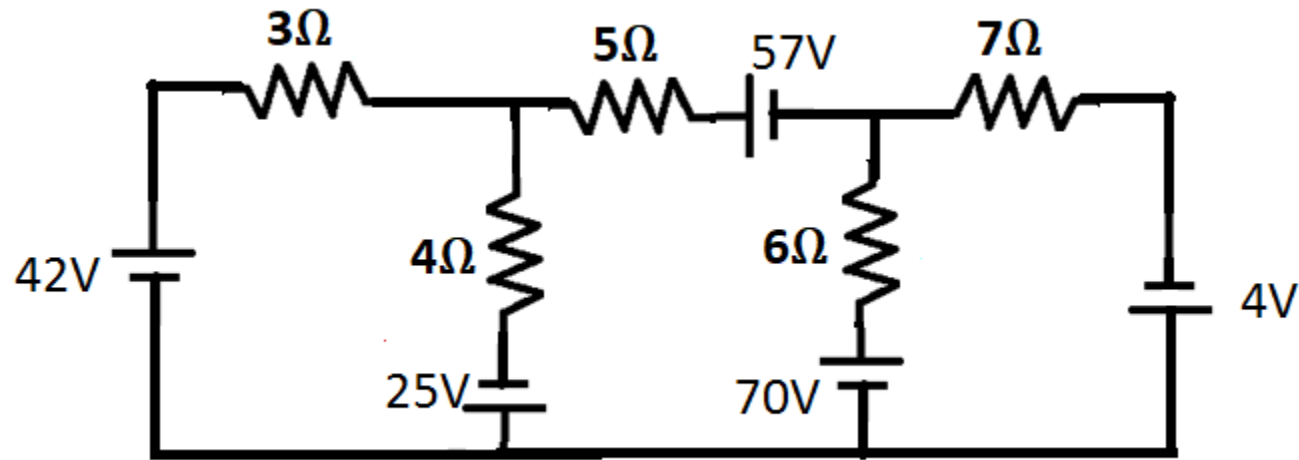
Question:

Obtain current through 6Ω resistor using Mesh Analysis.



Mesh Analysis – Numerical Example

Solution:

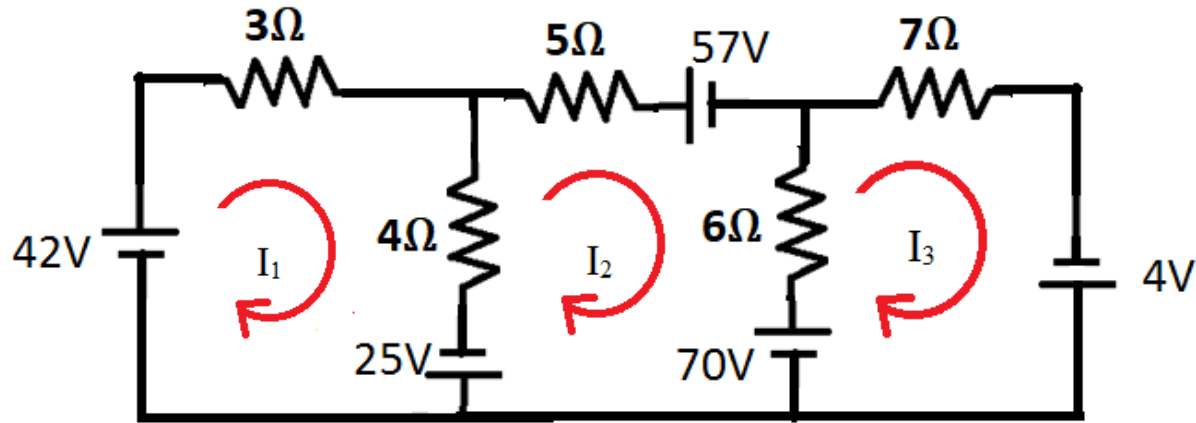

Number of Meshes = 3


$$\text{KVL (Mesh 1)} : -3I_1 - 4(I_1 - I_2) + 25 + 42 = 0 \quad \text{---- (1)}$$

$$\text{KVL (Mesh 2)} : -5I_2 - 57 - 6(I_2 - I_3) - 70 - 25 - 4(I_2 - I_1) = 0 \quad \text{---- (2)}$$

$$\text{KVL (Mesh 3)} : -7I_3 + 4 + 70 - 6(I_3 - I_2) = 0 \quad \text{---- (3)}$$

Mesh Analysis – Numerical Example

Solution (Continued..):

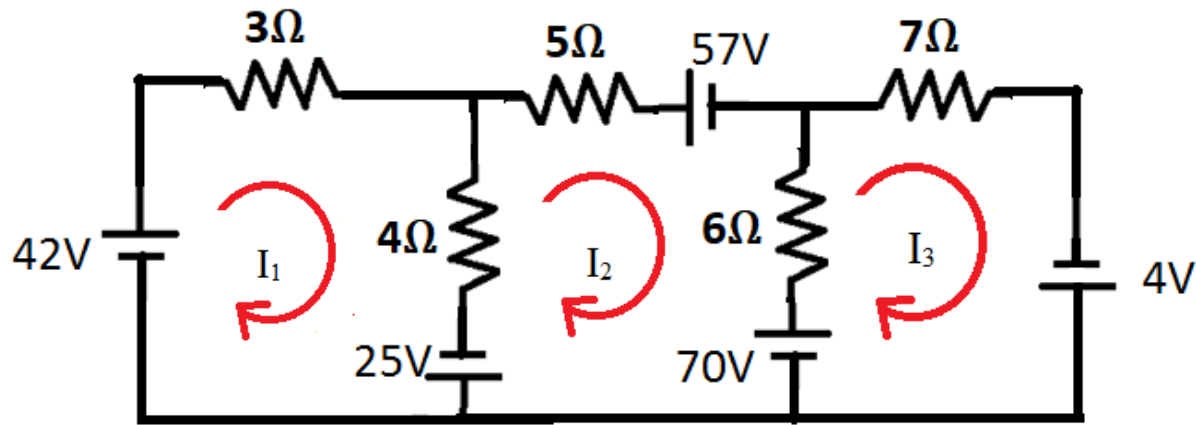


Solving the simultaneous equations (1), (2) & (3),

$$I_1 = 5A \ ; \ I_2 = -8A \ ; \ I_3 = 2A$$

Current through 6Ω resistor = $(I_2 \sim I_3) = (I_3 - I_2) = 10A$

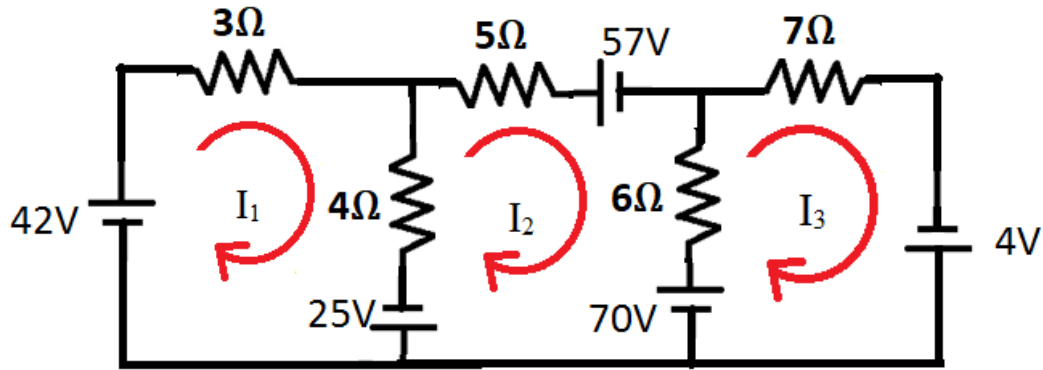Mesh Analysis – Writing KVLs by Direct Inspection



- Coefficient of same mesh current = Sum of all resistances in that mesh.
- Coefficient of other mesh current = Negative of Sum of all common resistances between the meshes.

$$\text{KVL (Mesh 1)} : 7I_1 - 4I_2 - 0I_3 = +25 + 42 \quad \text{---- (1)}$$

$$\text{KVL (Mesh 2)} : -4I_1 + 15I_2 - 6I_3 = -57 - 70 - 25 \quad \text{---- (2)}$$

$$\text{KVL (Mesh 3)} : 0I_1 - 6I_2 + 13I_3 = +4 + 70 \quad \text{---- (3)}$$

Text Book & References

Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11th Edition, Pearson Education, 2012.

Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8th Edition, McGraw-Hill, 2012.



THANK YOU

Vadhiraj K P P

Department of Electrical & Electronics Engineering

vadhirajkpp@pes.edu