



# **ELEMENTS OF ELECTRICAL ENGINEERING (UE24EE141B)**

---

**Vadhiraj K P P**

Department of Electrical Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

---

## Unit 2 – Lecture 36 - Numerical Examples on Series-Parallel AC Circuits

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

## Numerical Example 3


---

### Question:

A voltage of 200 V is applied to a pure resistor (R), a pure capacitor, C and a lossy inductor coil with resistance of  $100\ \Omega$ , all of them connected in parallel. The total current is 2.45 A, while the component currents are 1.5, 2.0 and 1.2 A respectively. Find the total power factor and also the power factor of the coil. Also find the total active and reactive power.

## Numerical Example 3

**Solution:**

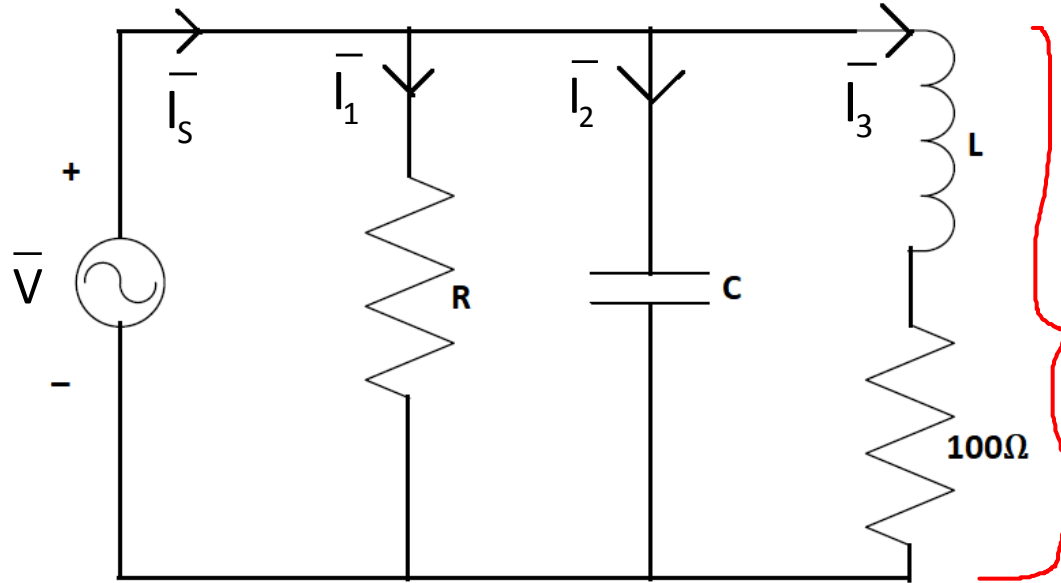

Let us consider supply voltage as reference


$$\Rightarrow \bar{V} = 200 \angle 0^\circ \text{ V}$$

Therefore,  $\bar{I}_1 = 1.5 \angle 0^\circ \text{ A}$  ;  $\bar{I}_2 = 2 \angle 90^\circ \text{ A}$

$$\text{In branch 3, } |Z_3| = \frac{200}{1.2} = 166.66\Omega$$

## Numerical Example 3

**Solution:**

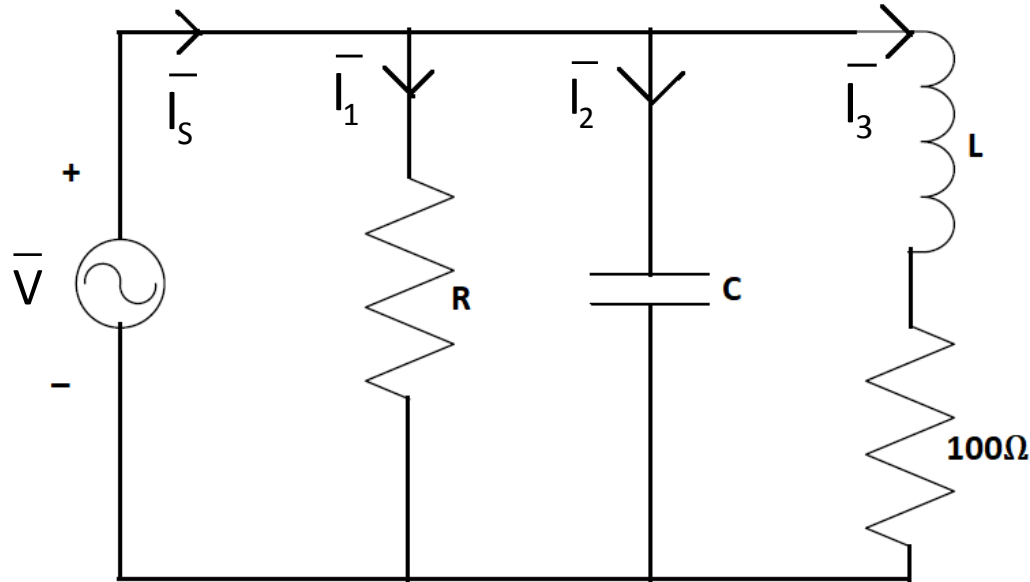

Therefore,  $\phi_3 = \cos^{-1}\left(\frac{r_3}{|Z_3|}\right) = 53.13^\circ \Rightarrow \bar{I}_3 = 1.2 \angle -53.13^\circ \text{ A}$


Hence,  $\bar{I}_s = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 2.45 \angle 25.1^\circ \text{ A}$

Phase Angle of the network =  $\phi = \angle \bar{V} - \angle \bar{I}_s = -25.1^\circ$

Overall Power factor =  $\cos \phi = 0.905$  Lead

## Numerical Example 3

**Solution:**

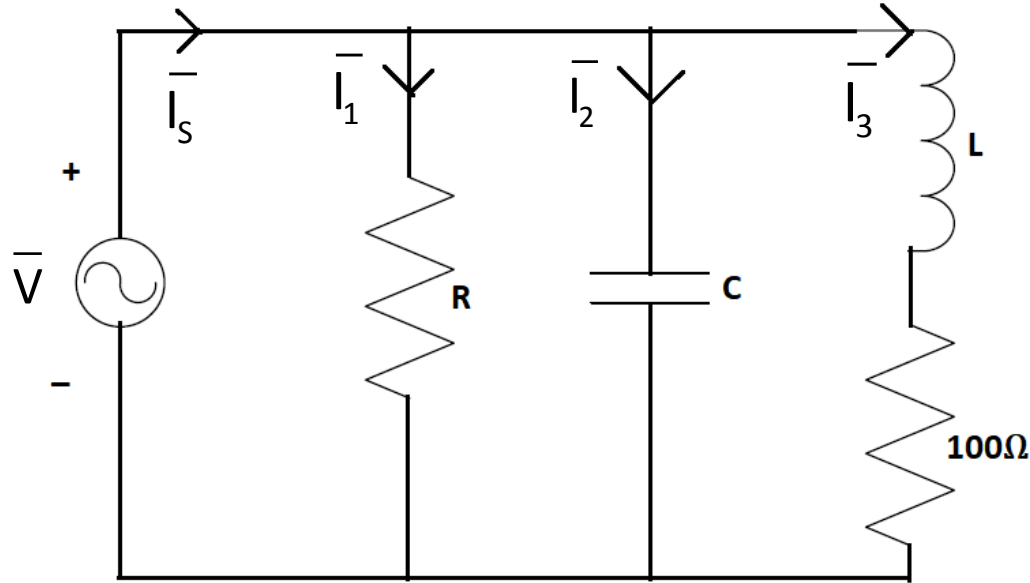

Power factor of the coil =  $\cos\phi_3 = 0.6$  Lag

Total Active Power,  $P_T = V \cdot I_S \cdot \cos\phi = 443.45\text{W}$

Total Reactive Power,  $Q_T = V \cdot I_S \cdot \sin\phi = -207.85 \text{ VAR}$

## Numerical Example 4


---

### Question:

The load connected across an AC supply consists of a heating load of 15KW, a motor load of 40KVA at 0.6 lag and a load of 20KW at 0.8 lag. Calculate the total power drawn from the supply in (KW and KVA) and its power factor. What would be the KVAR rating of a capacitor to bring the power factor to unity and how must the capacitor be connected?

## Numerical Example 4

**Solution:**

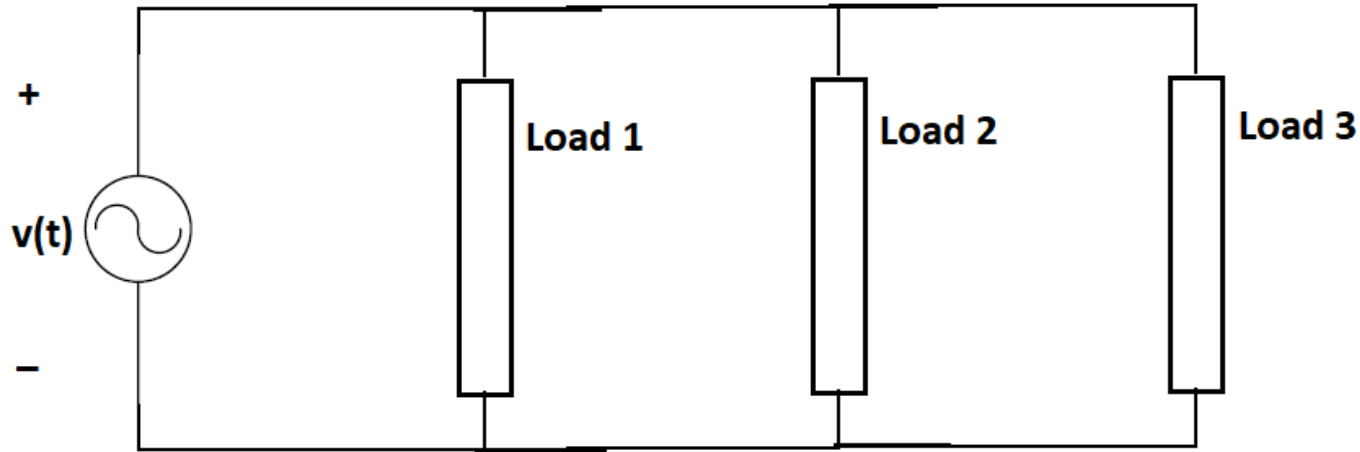

Load 1 : Heating Load  $\Rightarrow$  Resistive  $\Rightarrow \cos\phi_1 = 1$

$P_1 = 15\text{KW}$  (given)


$Q_1 = 0$

$S_1 = \sqrt{P_1^2 + Q_1^2} = 15\text{KVA}$



## Numerical Example 4

**Solution:**

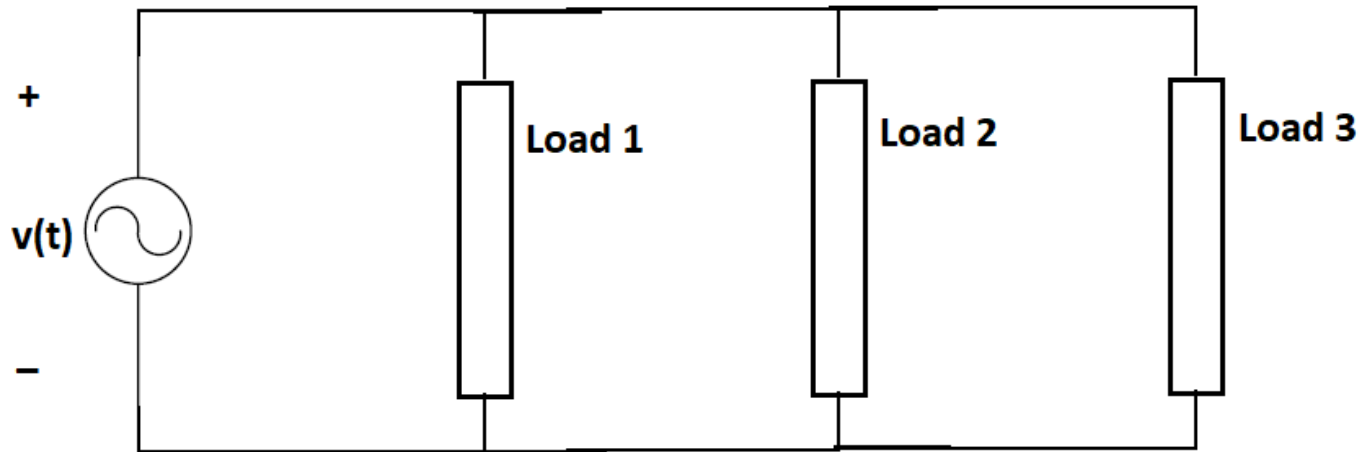

Load 2 : Motor Load  $\Rightarrow$  Inductive


$S_2 = 40\text{KVA}$  &  $\cos\phi_2 = 0.6$  Lag (given)

$P_2 = S_2 \cos\phi_2 = 24\text{KW}$

$Q_2 = \sqrt{S_2^2 - P_2^2} = 32\text{KVAR}$

## Numerical Example 4

**Solution:**

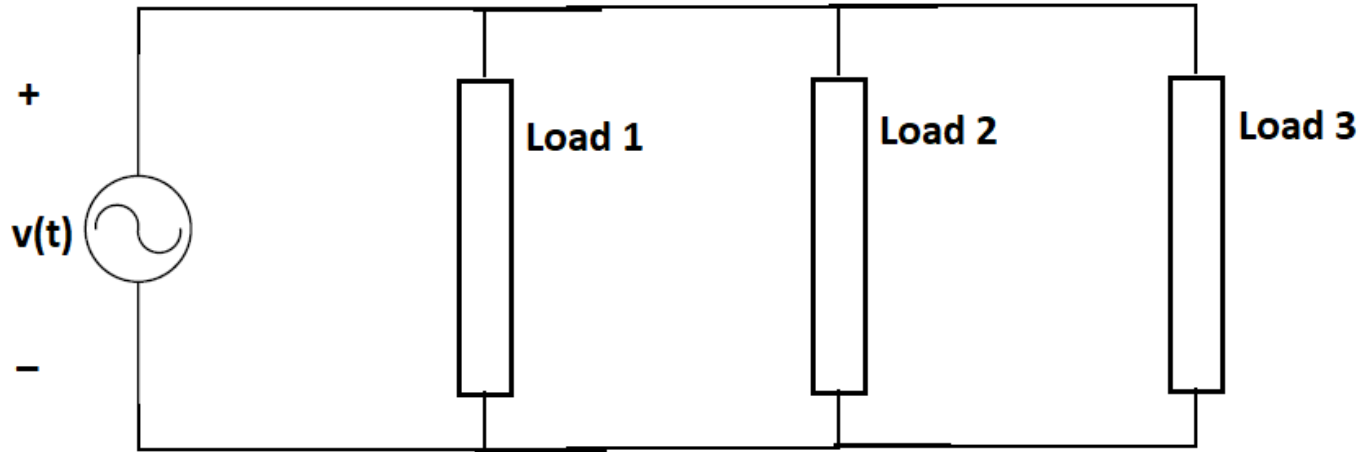

Load 3 : Inductive Load


$P_3 = 20\text{KW}$  &  $\cos\phi_3 = 0.8$  Lag (given)

$$S_3 = \frac{P_3}{\cos\phi_3} = 25\text{KVA}$$

$$Q_3 = \sqrt{S_3^2 - P_3^2} = 15\text{KVAR}$$

## Numerical Example 4

**Solution:**

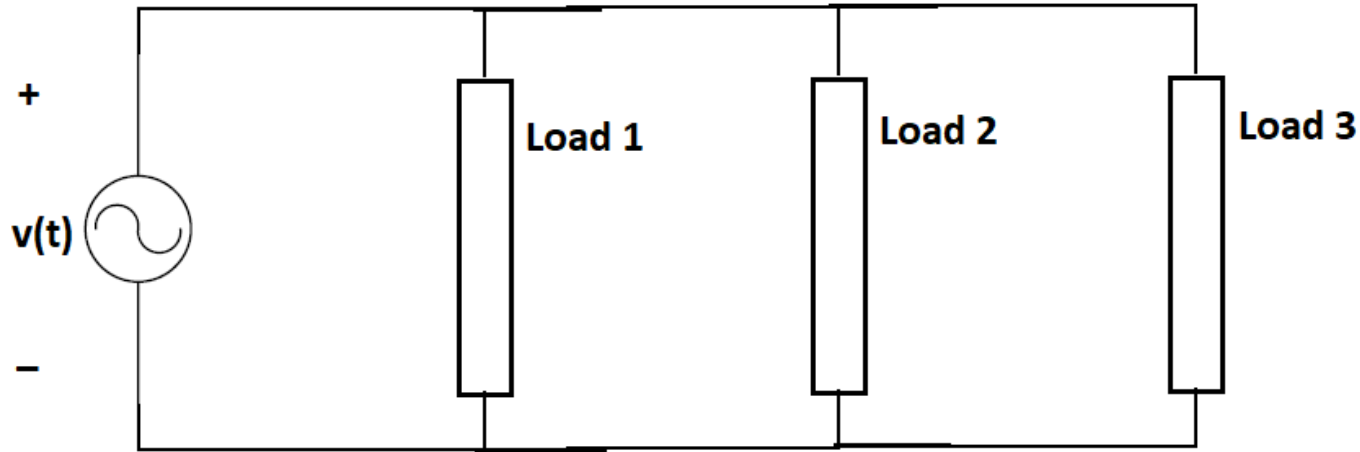

Net Active Power,  $P_T = P_1 + P_2 + P_3 = 59\text{KW}$

Net Reactive Power,  $Q_T = Q_1 + Q_2 + Q_3 = 47\text{KVAR}$

Net Apparent Power,  $S_T = \sqrt{P_T^2 + Q_T^2} = 75.43\text{KVA}$

To make overall power factor unity, net reactive power must be zero. Hence, connect a capacitor of rating 47KVAR in parallel to achieve this.

## Numerical Example 5

### Question:

b) An AC circuit has two branches A & B connected in parallel across a 230V, 50 Hz supply. Branch A consists of a coil with inductance 100mH and resistance  $10\Omega$ . Branch B takes a leading current from the supply. If the total power drawn from the source is 1KW and the overall power factor is 0.6 Lag, determine the resistance and capacitance in branch B.

$C = 99 \mu F$

## Numerical Example 3

c)	The power consumed in the inductive load is 5 kW at 0.6 lagging power factor .The input voltage is 230 V, 50 Hz. Find the value of the capacitor C which must be placed in parallel, such that the resultant power factor of the input current improves to 0.8 lagging.	8
----	---	---

c)	<p>A single-phase AC network consists of impedances <math>Z_1</math> and <math>Z_2</math> connected in parallel. This parallel combination is connected in series with another impedance <math>Z_3</math>. If this network is connected across a 200V, 50Hz AC supply &amp; the supply current is 10A at a lagging power factor of 0.6, determine</p> <ul style="list-style-type: none"><li>i) Impedance <math>Z_2</math> if <math>Z_1 = (15+j20) \Omega</math> &amp; <math>Z_3 = (6+j8) \Omega</math></li><li>ii) Branch currents in <math>Z_1</math> and <math>Z_2</math></li><li>iii) Reactive Powers in <math>Z_1</math> and <math>Z_2</math></li></ul>	8M
----	---	----



**THANK YOU**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**