



# ELEMENTS OF ELECTRICAL ENGINEERING

## UE24EE141B

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

## UE24EE141B

---

### Lecture 15 - Numerical Examples on Superposition Theorem


**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

## Numerical Example 1
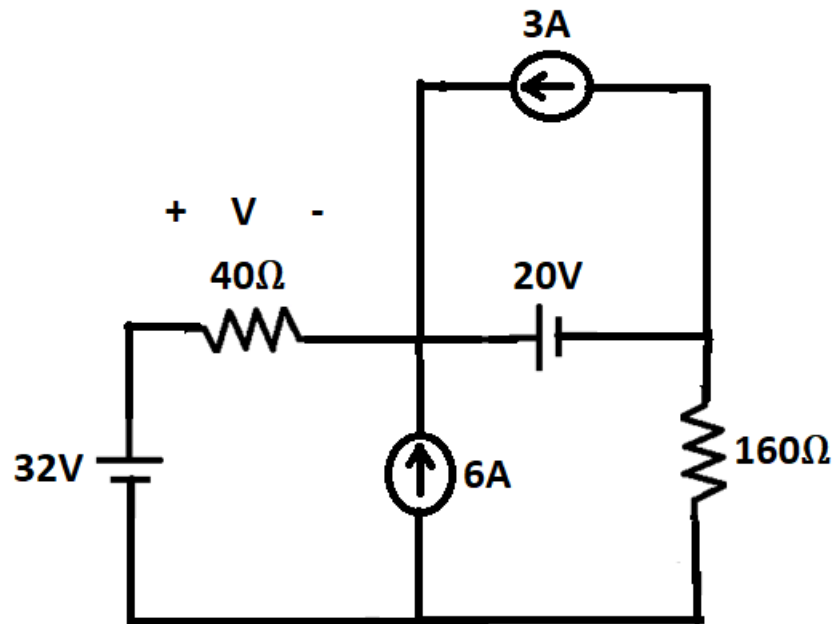
### Question:


Obtain voltage 'V' using Superposition Theorem.



## Numerical Example 1


### Solution :

Considering 32V source alone,

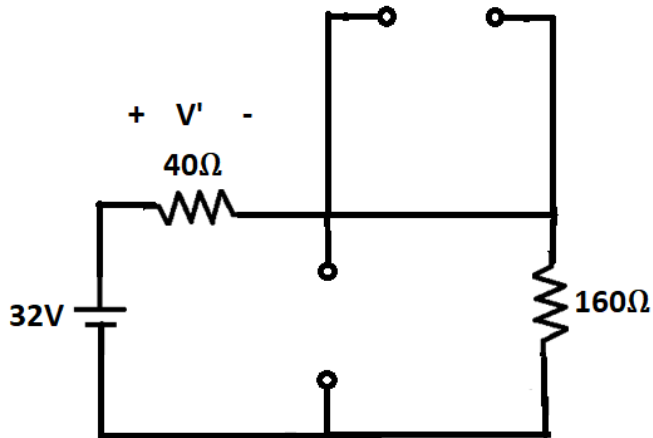

$$V' = 32V * \frac{40\Omega}{200\Omega} = 6.4V$$




(Voltage Division rule)

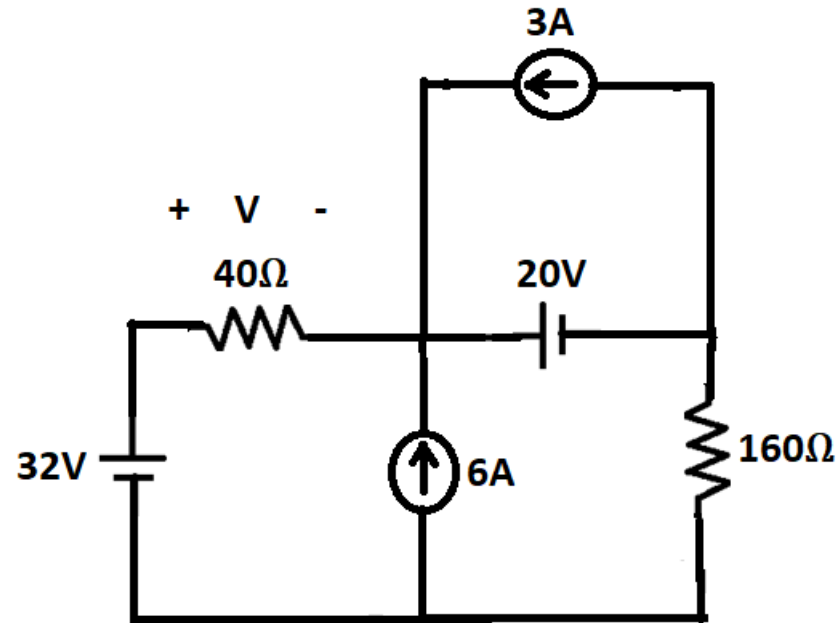

## Numerical Example 1

**Solution (Continued..)** :

Considering 6A source alone,

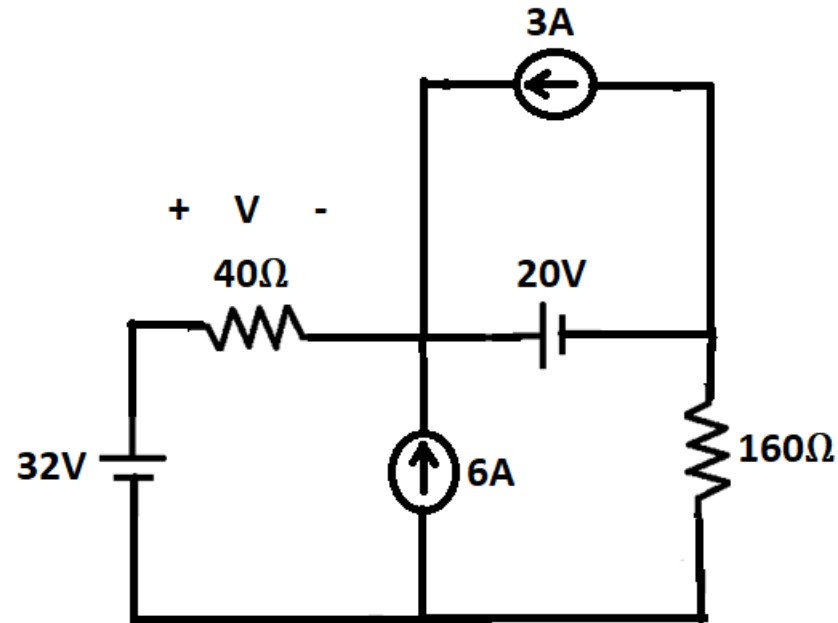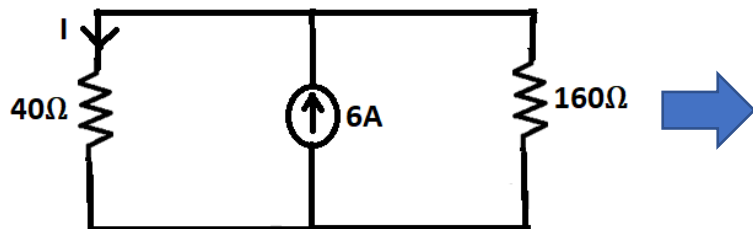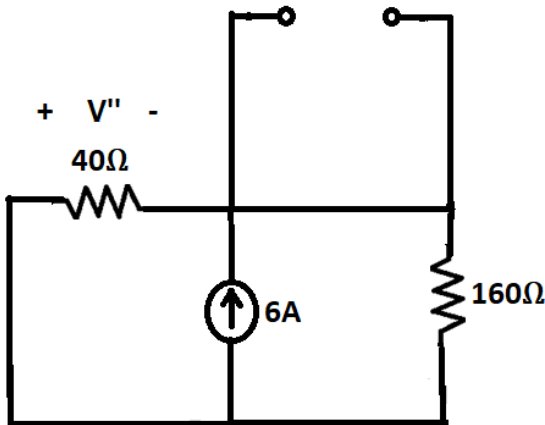




$$I = 6A * \frac{160\Omega}{200\Omega} = 4.8A$$

$$V'' = -4.8A * 40\Omega = -192V$$

## Numerical Example 1

**Solution (Continued..)** :

Considering 20V source alone,

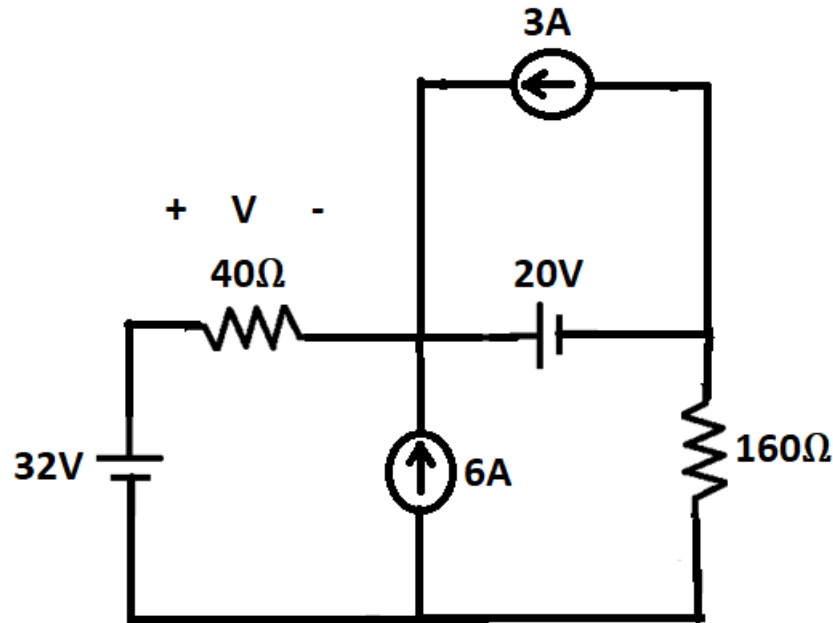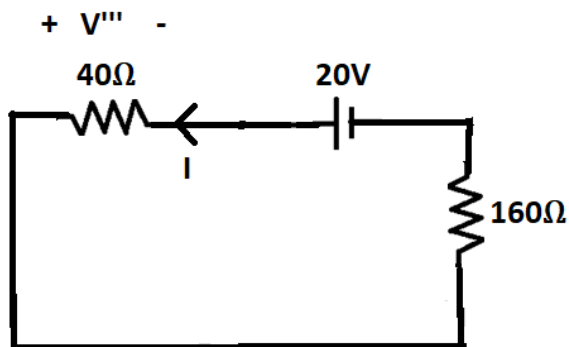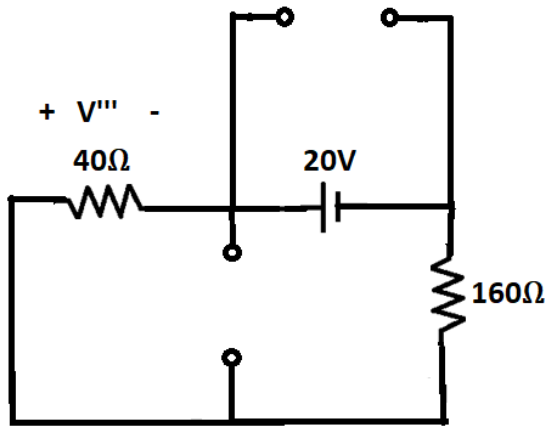


$$I = \frac{20V}{200\Omega} = 0.1A$$

$$V''' = -0.1A * 40\Omega = -4V$$


## Numerical Example 1

**Solution (Continued..)** :

Considering 3A source alone,

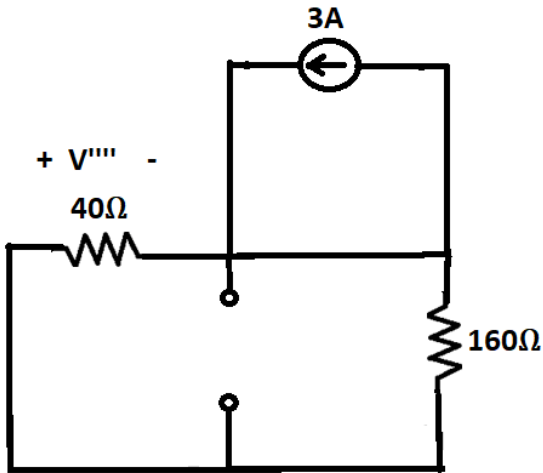

$$V'''' = 0$$

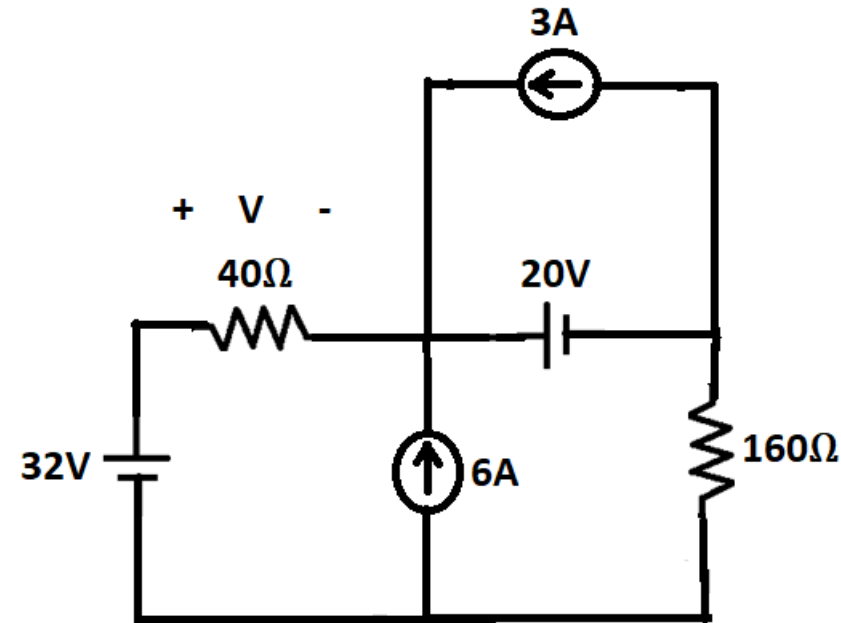

By Superposition Theorem,


$$V = V' + V'' + V''' + V'''' = -189.6V$$

## Numerical Example 2

---
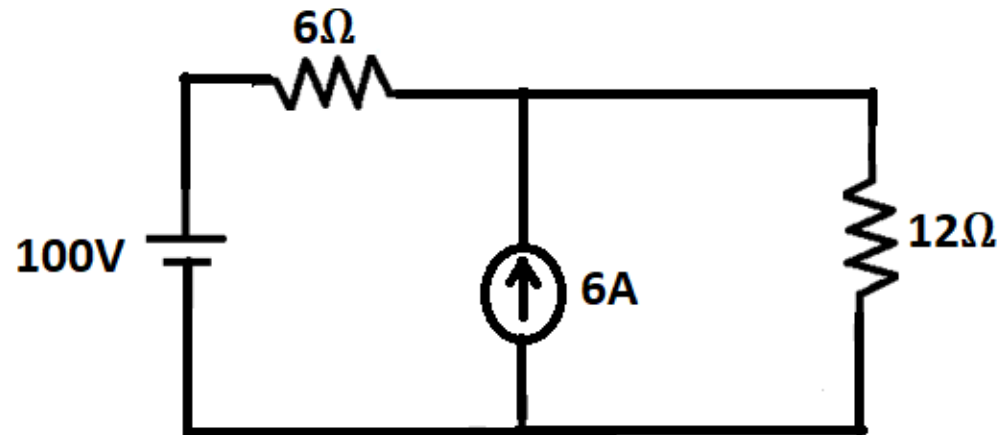
### Question:


Find the power absorbed by  $12\Omega$  resistor using Superposition Theorem.





## Numerical Example 2

**Solution :**

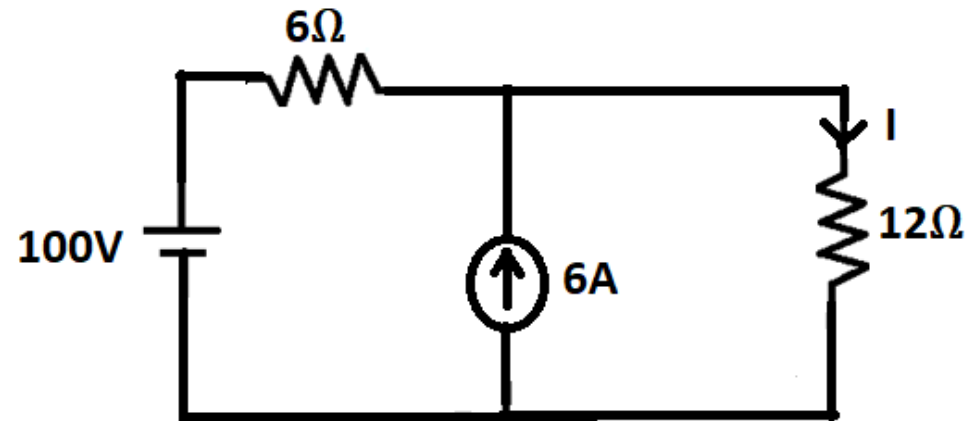


Let us consider individual current & Power responses due to 100V source acting alone as  $I'$  &  $P'$

Let us consider individual current & Power responses due to 6A source acting alone as  $I''$  &  $P''$

## Numerical Example 2

**Solution (Continued..) :**

Considering 100V source alone,

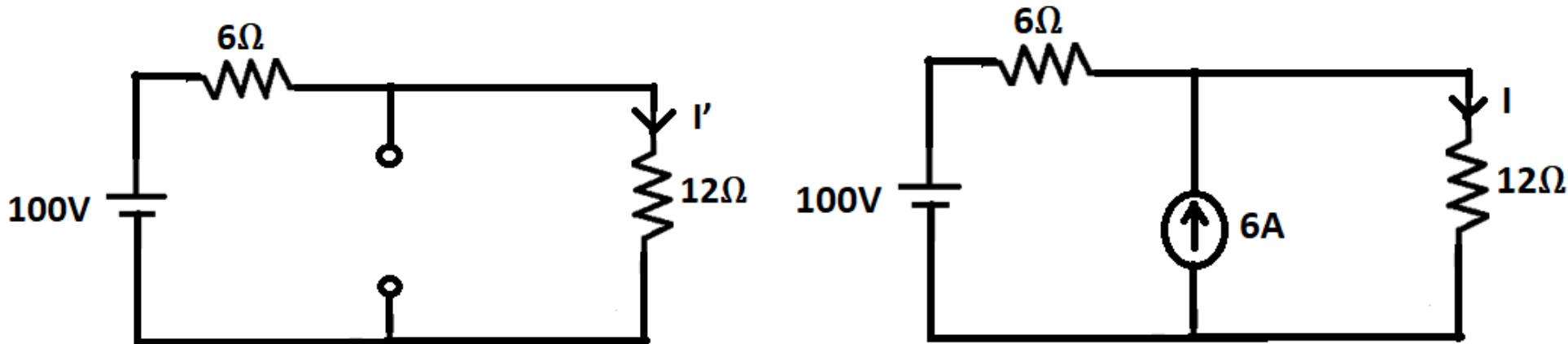


$$I' = \frac{100V}{18\Omega} = 5.56A \quad \& \quad P' = (I')^2 * 12 = 370.96W$$


## Numerical Example 2

**Solution (Continued..) :**

Considering 6A source alone,

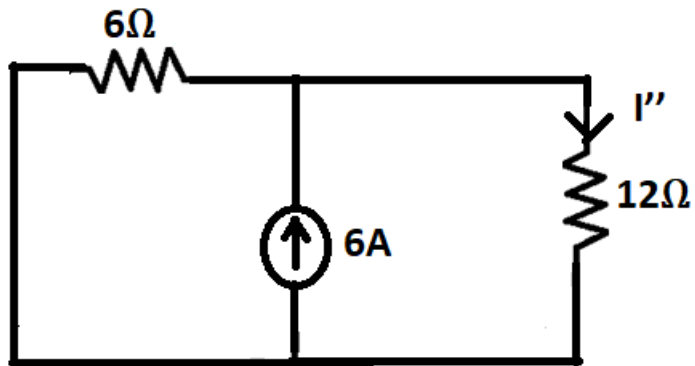
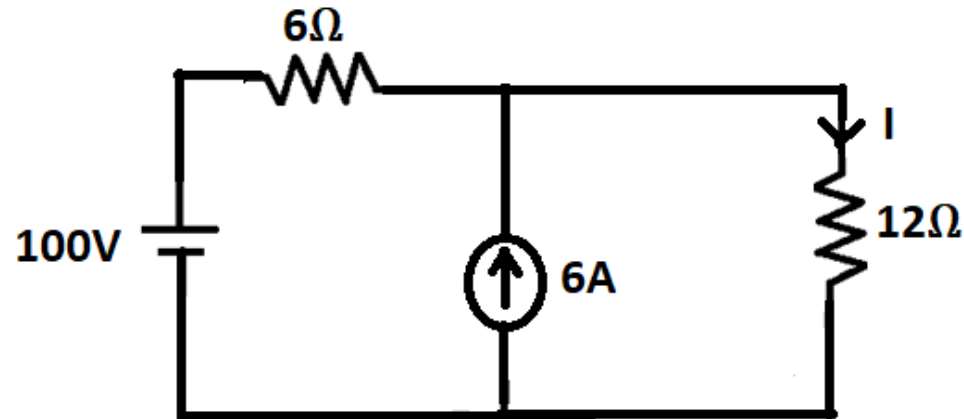
$$I'' = 6A * \frac{6\Omega}{18\Omega} = 2A \quad \& \quad P'' = (I'')^2 * 12 = 48W$$



## Numerical Example 2

---

### **Solution (Continued..) :**

By Superposition, current in  $12\Omega$  resistor =  $I = I' + I'' = 7.56A$

Hence, Power absorbed by  $12\Omega$  resistor =  $I^2 * 12 = 685.84W$

Adding the individual Power responses,  $P' + P'' = 418.96W$ , which is not equal to the actual power absorbed.


Hence, individual power responses cannot be superposed to get total power because power is a quadratic term.

Thus, to get total power response, apply superposition principle to get total current or total voltage & using that find the power.

## Numerical Example 1

b) Determine the current through  $6\Omega$  resistor in the given network using Superposition Theorem.


6M

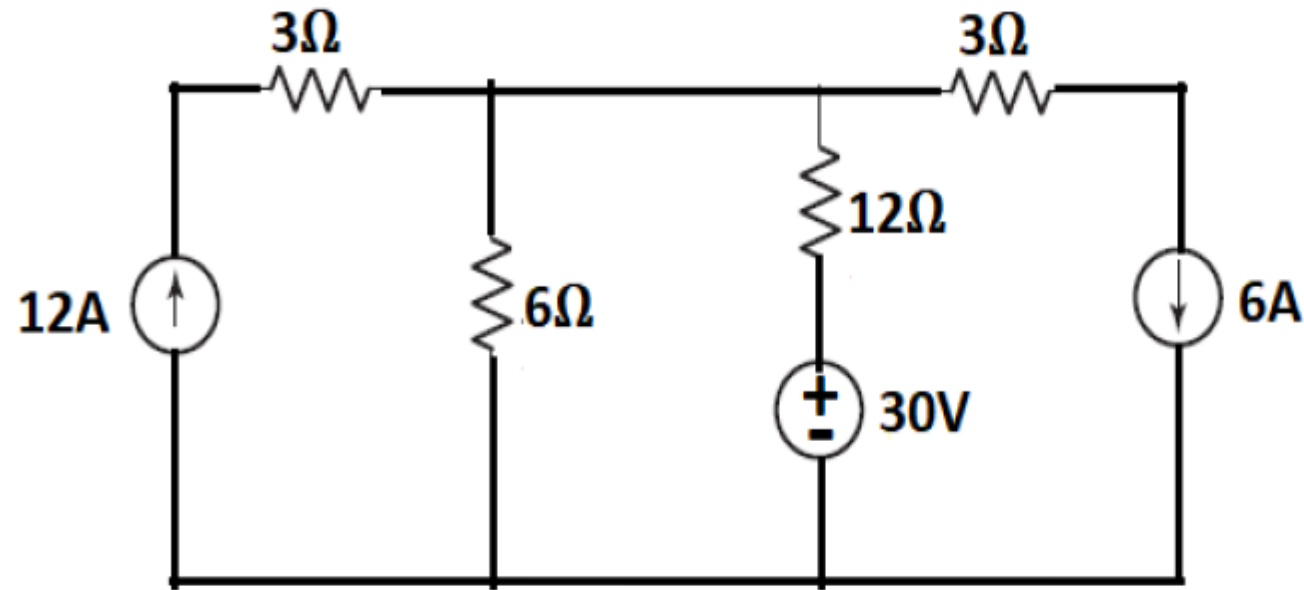

## Numerical Example 1

- b) Determine the current through  $2\Omega$  resistor in the given network using Superposition Theorem.

6M

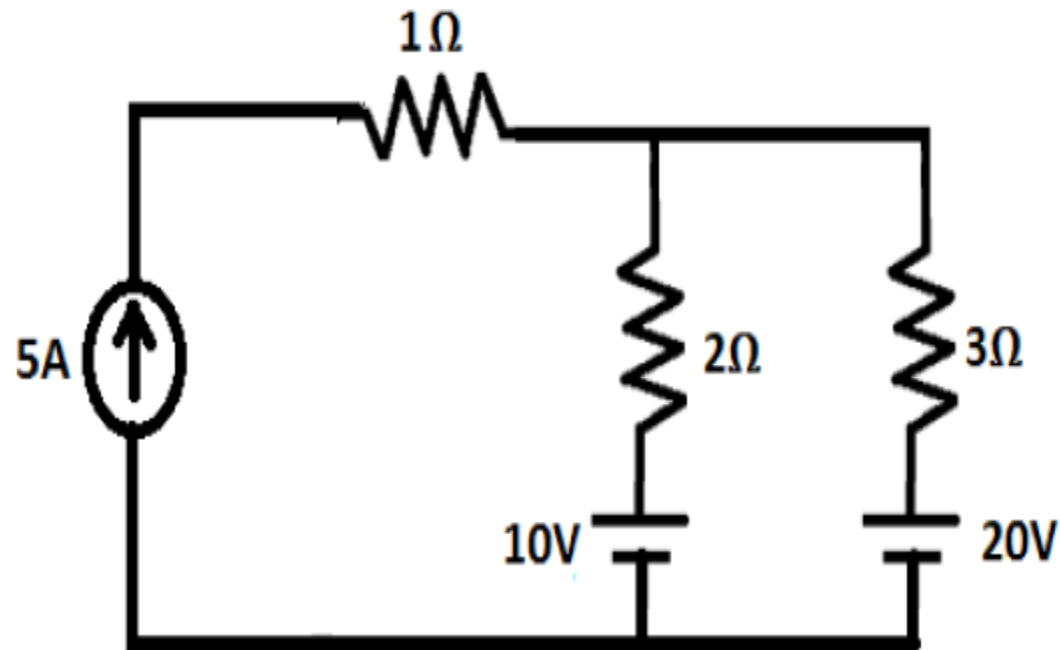

## Text Book & References

---

### Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11<sup>th</sup> Edition, Pearson Education, 2012.

### Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8<sup>th</sup> Edition, McGraw-Hill, 2012.



**THANK YOU**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**