



# ELEMENTS OF ELECTRICAL ENGINEERING

## UE24EE141B

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

# **ELEMENTS OF ELECTRICAL ENGINEERING**

## **UE24EE141B**

---

### **Star Delta Transformations**


**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

## Star Delta Transformations – Numerical Example 3


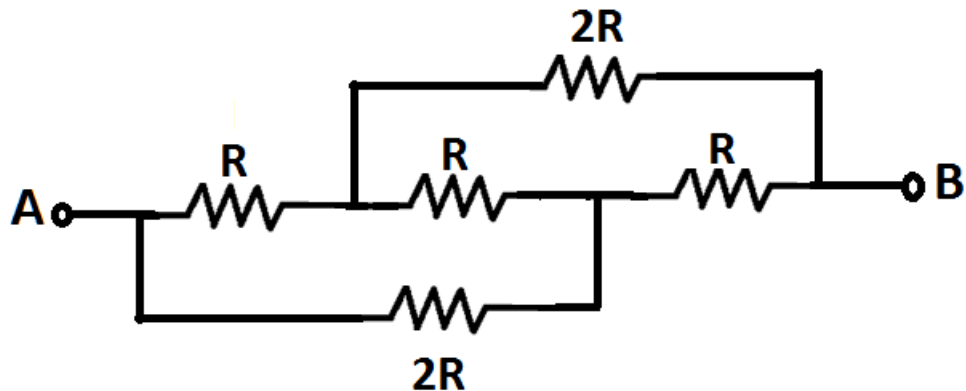
### Question:

Find the equivalent resistance between the terminals A & B in the given network.



## Star Delta Transformations – Numerical Example 3

**Solution:**

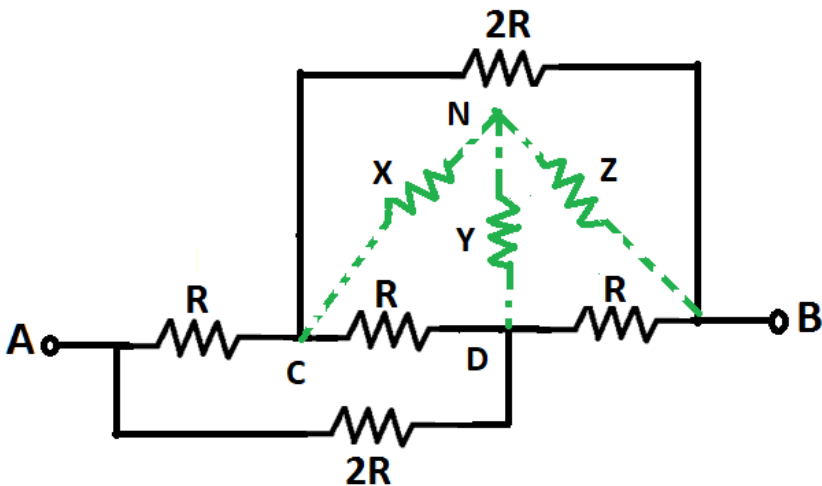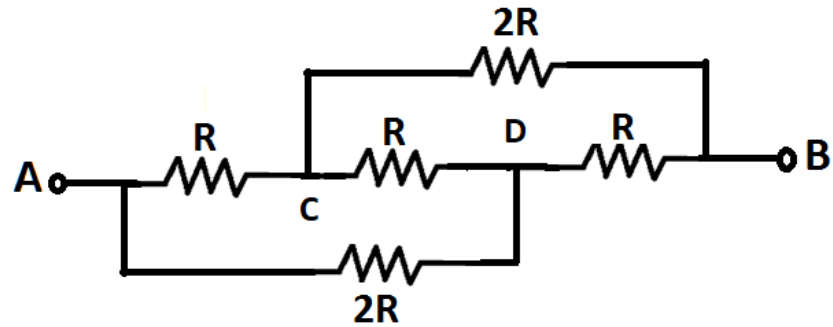




$$X = \frac{R * 2R}{(R + 2R + R)} = \frac{R}{2} \Omega$$

$$Y = \frac{R * R}{(R + 2R + R)} = \frac{R}{4} \Omega$$

$$Z = \frac{R * 2R}{(R + 2R + R)} = \frac{R}{2} \Omega$$

## Star Delta Transformations – Numerical Example 3


Solution (Continued..) :

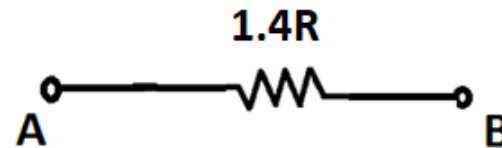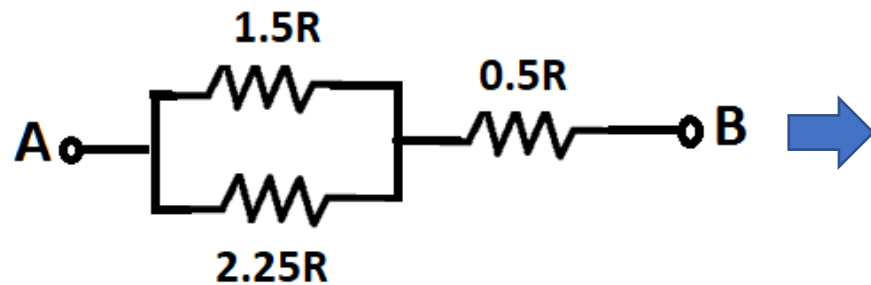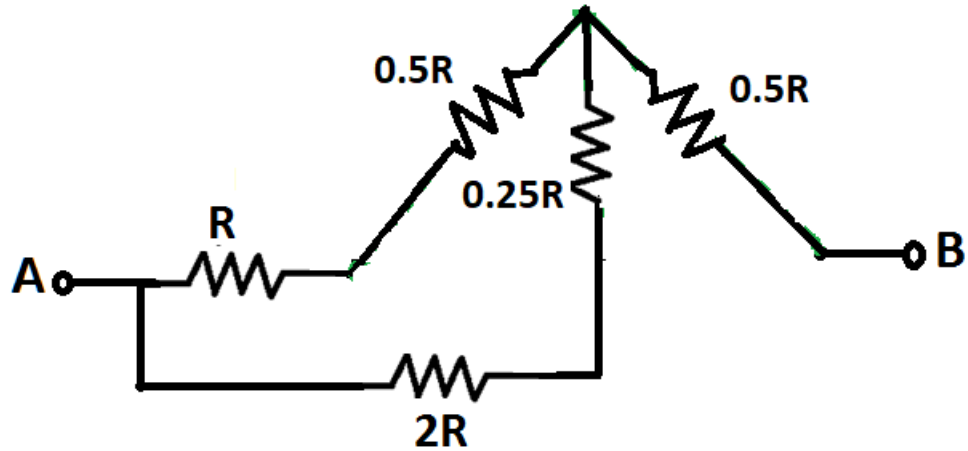

## Star Delta Transformations – Numerical Example 4


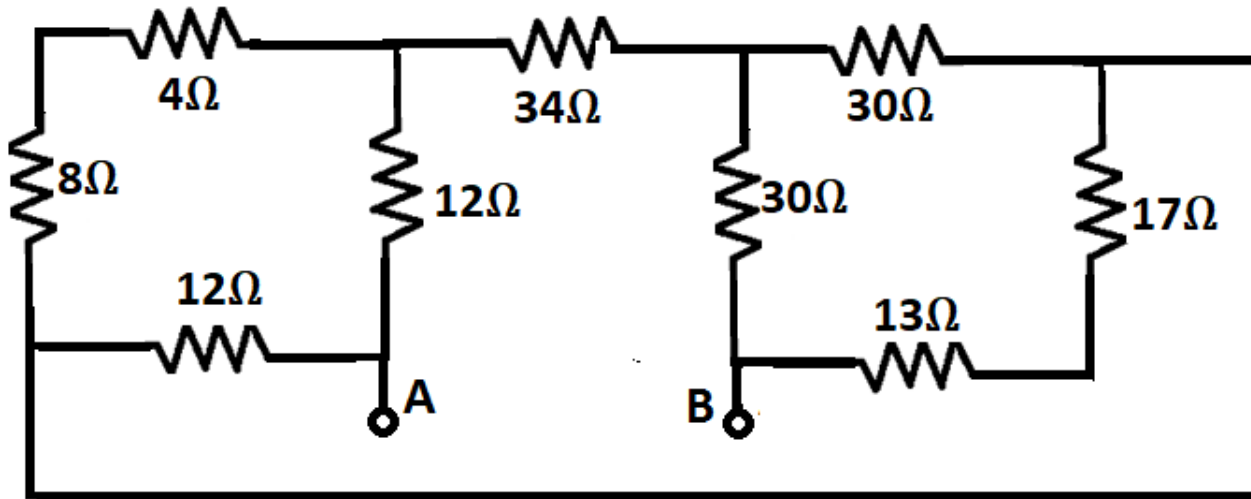
### Question:

Find the equivalent resistance between the terminals A & B in the network shown.







## Star Delta Transformations – Numerical Example 4

**Solution:**

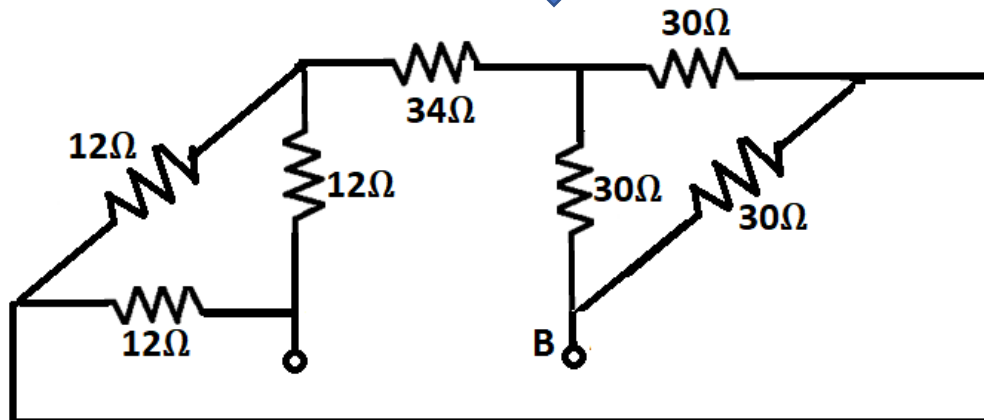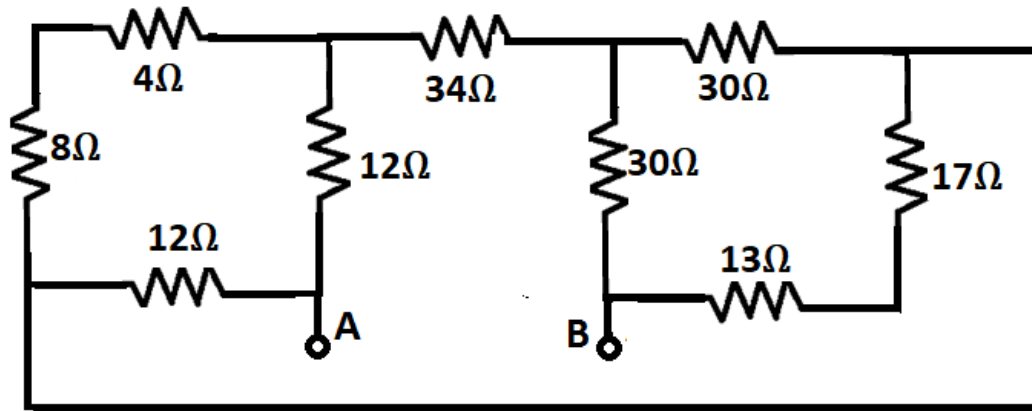

## Star Delta Transformations – Numerical Example 4

Solution (Continued..) :

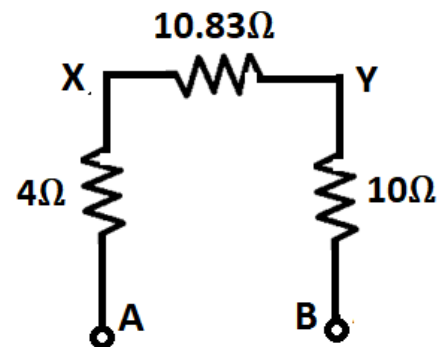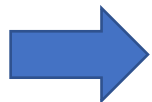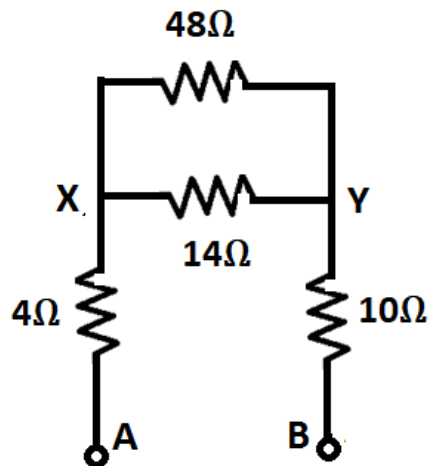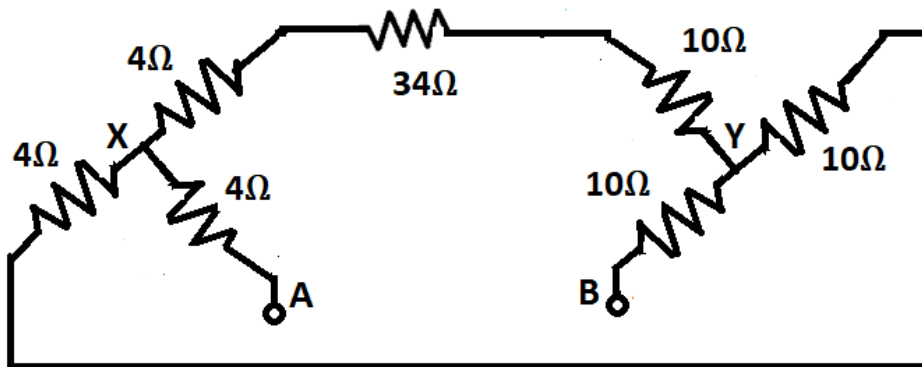


$$R_{AB} = 24.83\Omega$$



## Star Delta Transformations – Numerical Example 5

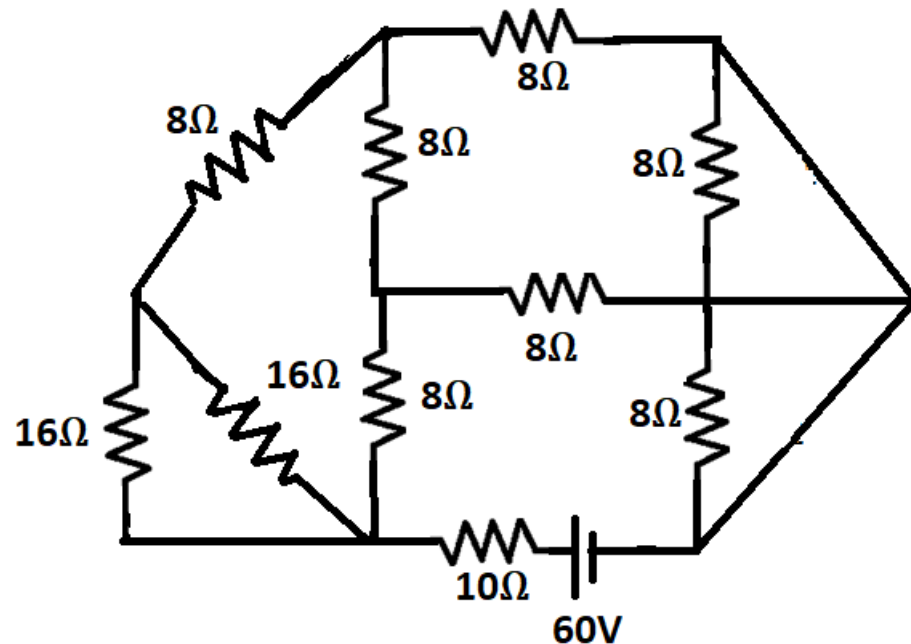
### Question:

Find the voltage drop across  $10\Omega$  resistor in the network shown.






## Star Delta Transformations – Numerical Example 5

**Solution:**

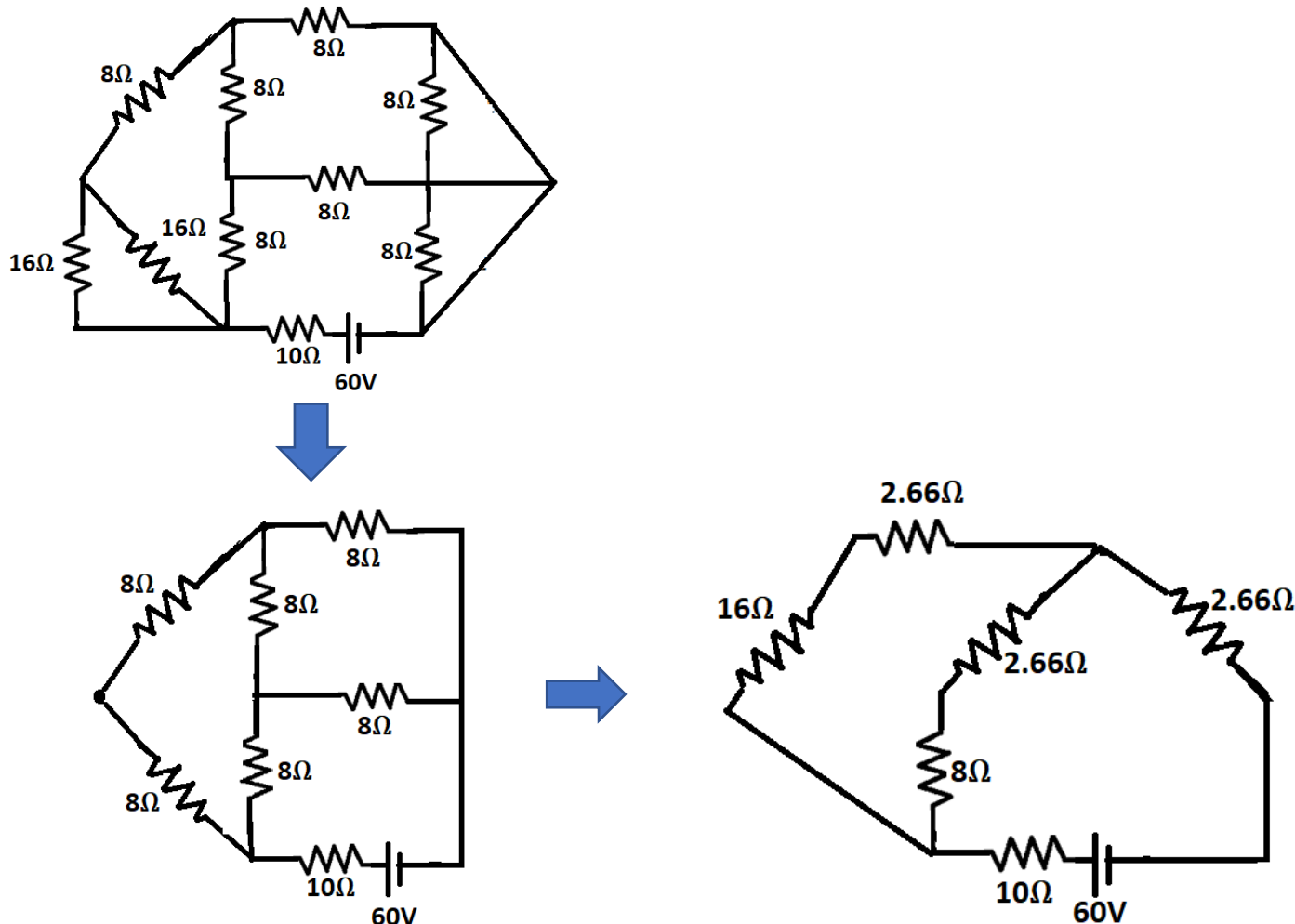


## Star Delta Transformations – Numerical Example 5

Solution (Continued..) :

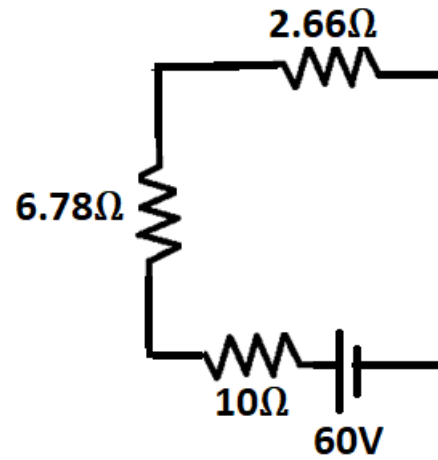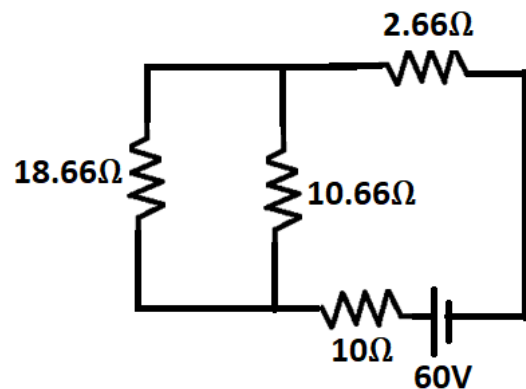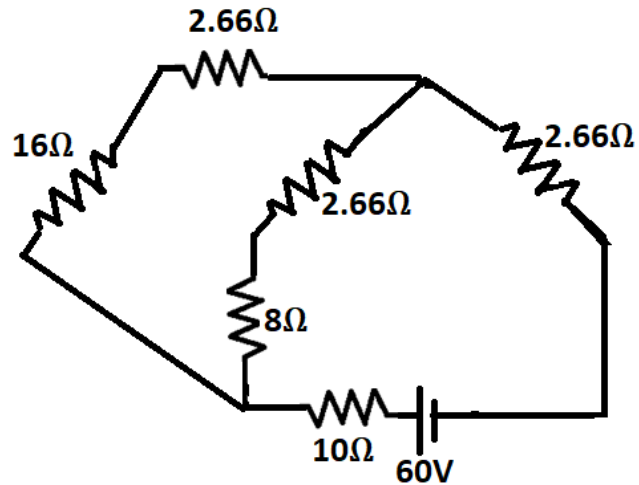

## Star Delta Transformations – Numerical Example 5


**Solution (Continued..) :**

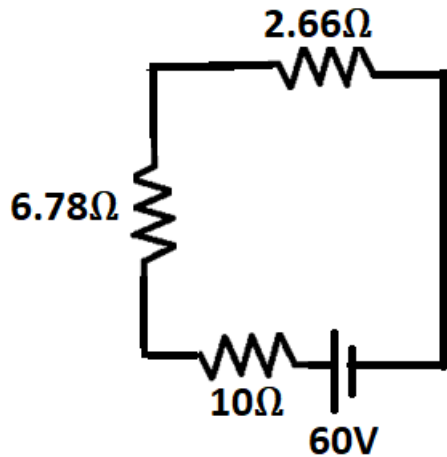


Current delivered by 60V source,  $I_S = \frac{60}{R_{eq}} = \frac{60}{19.44} = 3.086\text{A}$

Voltage drop across 10Ω resistor =  $I_S * 10 = 30.86\text{V}$
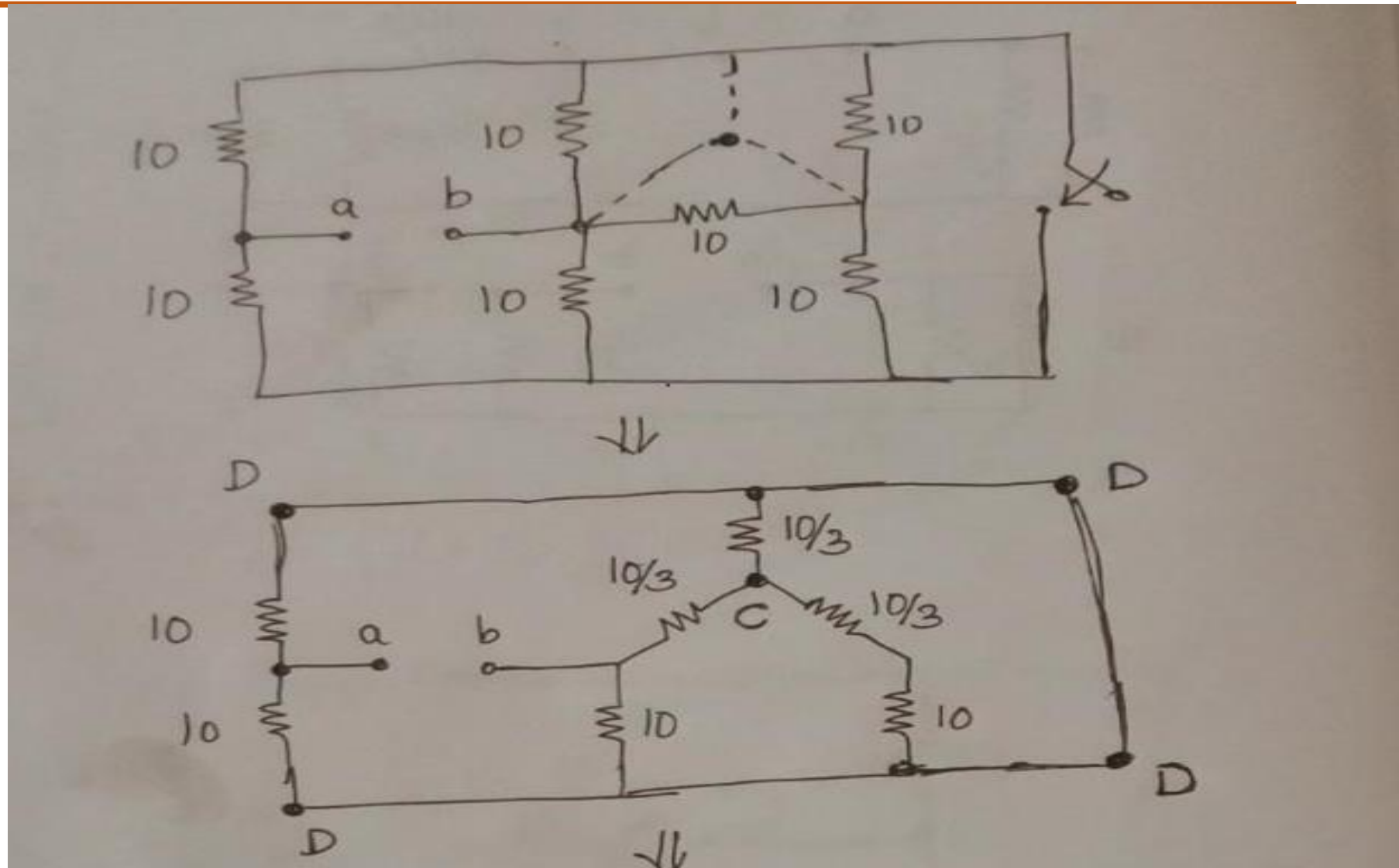
## Star Delta Transformations – Numerical Example 5


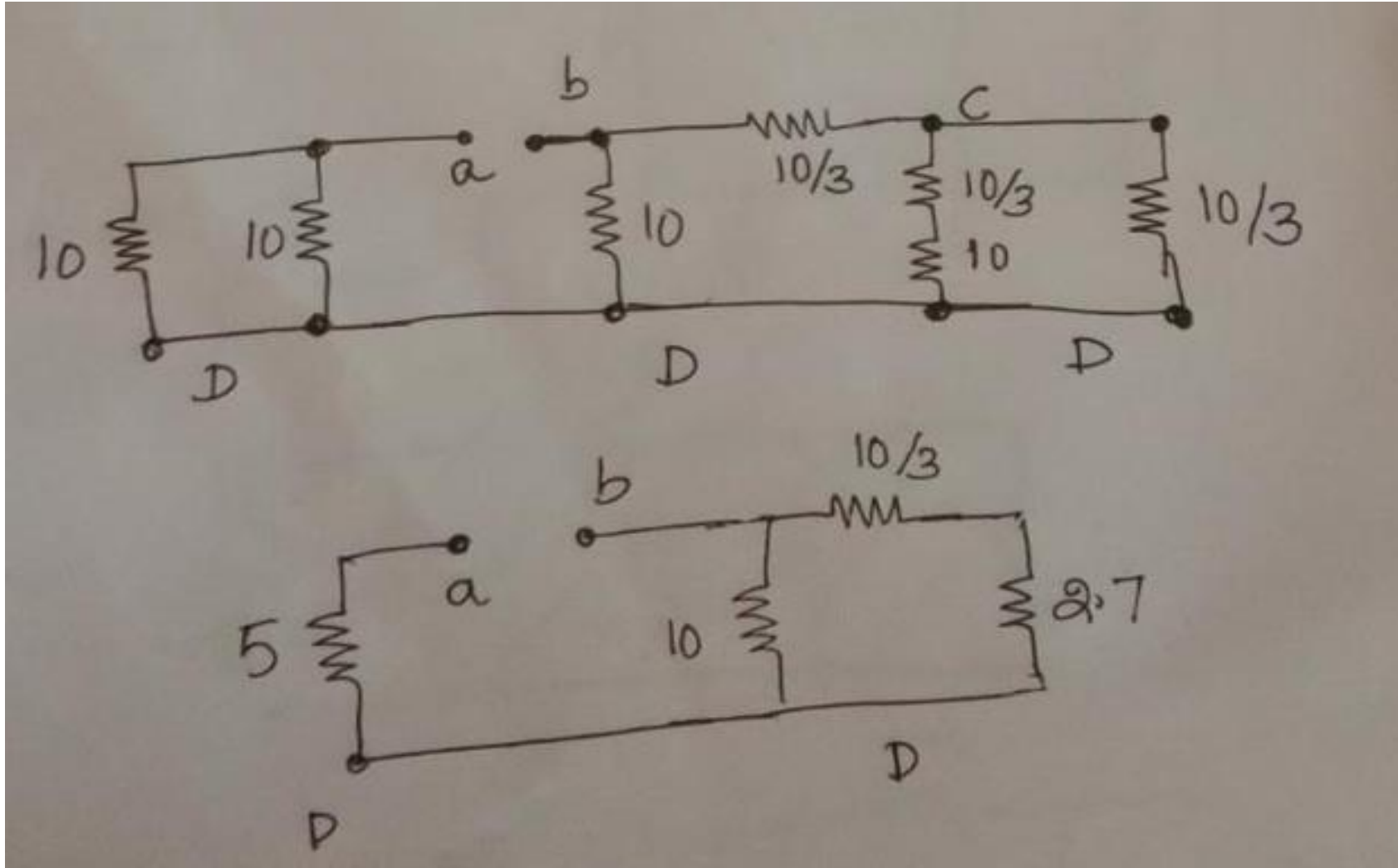
## Star Delta Transformations – Numerical Example 5



## Text Book & References

---

### Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11<sup>th</sup> Edition, Pearson Education, 2012.

### Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8<sup>th</sup> Edition, McGraw-Hill, 2012.



**THANK YOU**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**